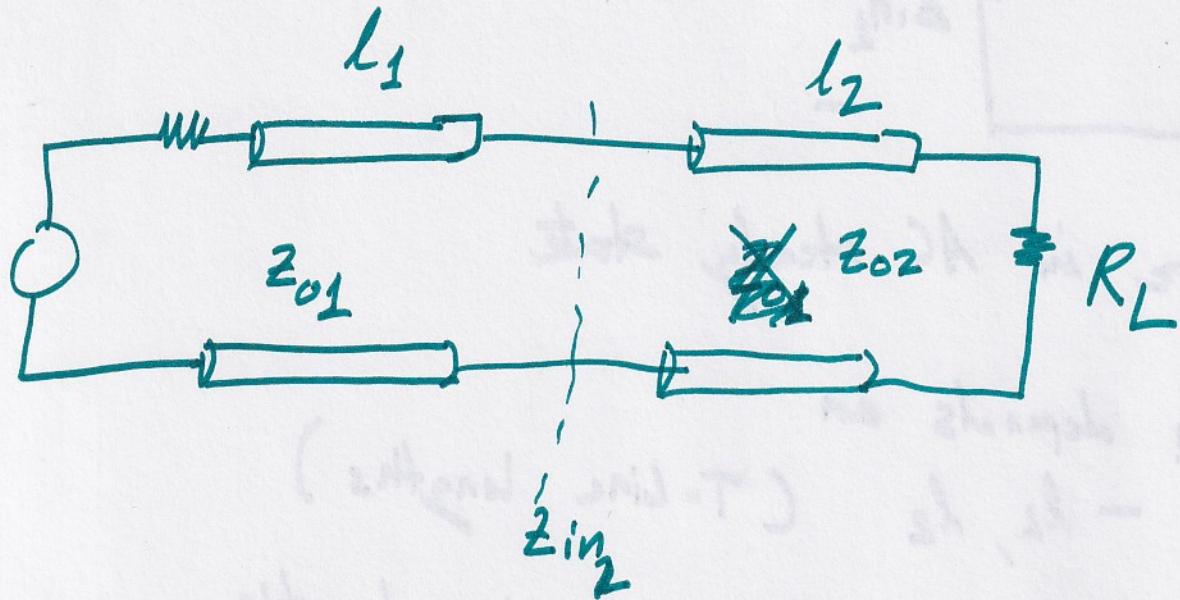


# Fields and Waves I LF


## Lossy Transmission Lines



We pay attention to the AC steady state point of view

$$Z_{in2} = Z_{02} \frac{Z_L + j Z_{02} \tan \beta l_2}{Z_{02} + j Z_L \tan \beta l_2}$$

so then we have

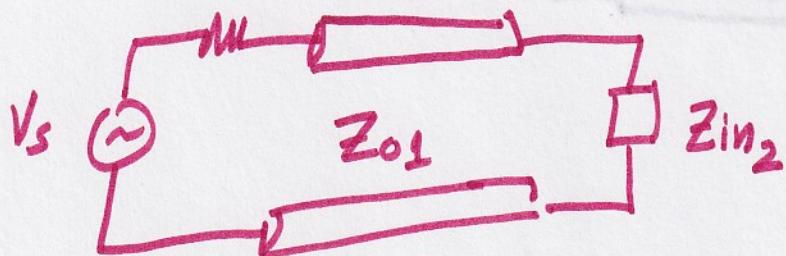


$$Z_{in1} = Z_{01} \frac{Z_{in2} + j Z_{01} \tan \beta l_1}{Z_{01} + j Z_{in2} \tan \beta l_1}$$

The effective load  
for Line 1

2


So then we have

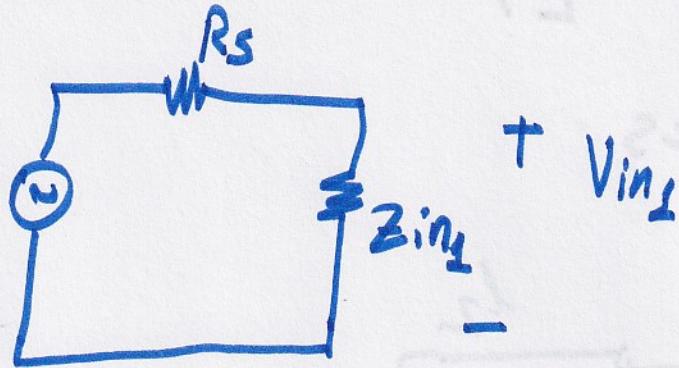

We are in AC steady state


$V_{in1}$  depends on

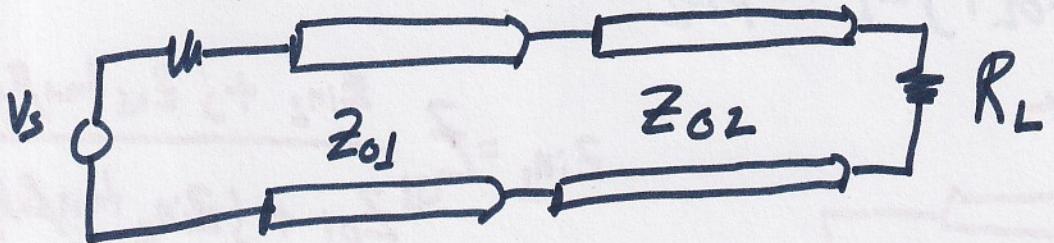- $l_1, l_2$  (T-Line lengths)
- $Z_{01}, Z_{02}$  (T-Line characteristic Impedance)
- $Z_L$  (Load)



# Pulse Analysis

$V_s$  turns on and sends a pulse

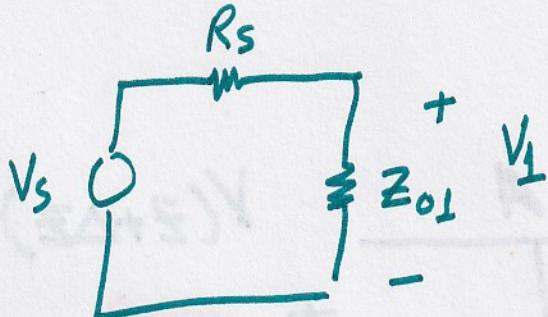


The Impedance seen is the characteristic Impedance  
(All that matters is the characteristic Impedance)

so the pulse hits  $Z_{01} - Z_{02}$  junction

→ Then you apply reflection concepts!

For  $T_1$  (T-line #1), the load is  $Z_{02}$


→ So at  $T_1$  end

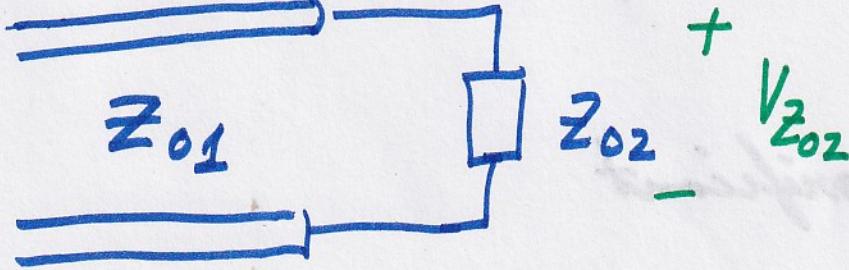

$V_{202}$  gets sent down  $T_2$   
(We will have reflection if  $\Gamma \neq 0$ )

# Lossy Lines

Lumped Parameter Model

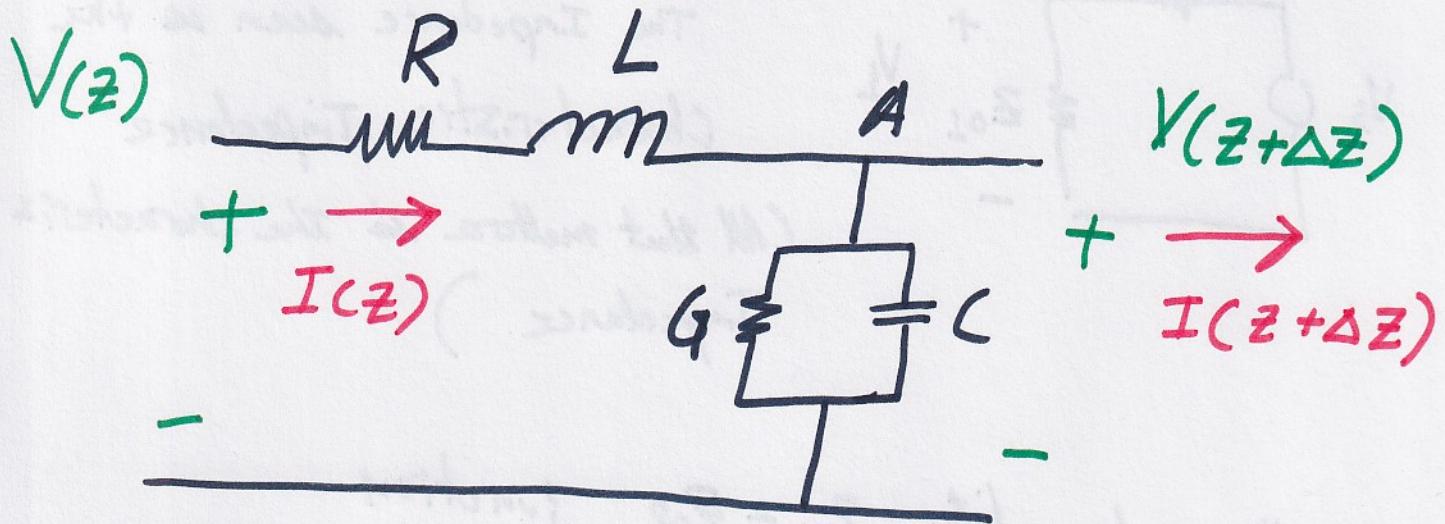

$$V = IR \quad (\Omega) R \rightarrow \text{resistance of the wires}$$

$$VG = I \quad \left( \frac{1}{\Omega} \right) G \rightarrow \text{Leakage current between wires}$$

Siemen

one section represents  $\Delta z$  meters

typically,

$R$  is significant

$G$  is negligible

How does  $R$ , and  $G$  affect the wave equation?

KCL at A

$$\frac{1}{\Delta z} [I(z + \Delta z) - I(z)] = C \frac{d}{dt} V(z + \Delta z) + V_G$$

current flows into A      current flows out of A into capacitor      current flowing into the conductance  
(or the current is actually into A, may not matter)

Let  $\Delta z \rightarrow$ , this becomes a derivative  
(This is the 'Idea')

$$\frac{d}{dz} I = C \frac{d}{dt} V + gV$$

$C/m$        $G/m$        $F$  conductance per meter  
Capacitance per meter

6 Let's do KVL

$$\frac{1}{\Delta z} \left[ V(z + \Delta z) - V(z) = V_L + V_R \right]$$
$$= L \frac{dI(z)}{dt} + I(z)R$$

Take  $\Delta z \rightarrow 0$

$$\frac{d}{dz} V(z) = l \frac{d}{dt} I(z) + r I(z)$$

↑

$L_m$

↑

$R_m$

Inductance per meter

Resistance per meter

Take the derivative

$$\frac{d^2}{dz^2} V = l \underbrace{\frac{d}{dz} \frac{d}{dt} I}_{\text{green bracket}} + r \frac{d}{dz} I$$

$$\begin{aligned} & \xrightarrow{\text{green bracket}} l \frac{d}{dt} \frac{d}{dz} I \quad (\text{we can do this, see} \\ & \quad \text{lecture 1}) \\ & \xrightarrow{\text{blue bracket}} lC \frac{d^2}{dt^2} V + gd \frac{d}{dt} V \end{aligned}$$

$$\downarrow$$

$$rc \frac{d}{dt} V + rgV$$

so the lossy wave equation

$$\frac{d^2}{dz^2} V = lc \frac{d^2}{dt^2} V + (rc + gl) \frac{d}{dt} V + rgV$$

So, skipping a lot of steps, we eventually get

$$V = V_0 e^{j(\omega t \pm \beta z)} \quad A function of t and z$$

$\uparrow$   
could have oscillation

This is the assumed solution to the wave equations.

Plug in the assumed "e<sup>jωt</sup>" into the differential equation.

$$\frac{d^2}{dz^2} V = -\omega^2 V + j\omega(rc + gl)V + \gamma V$$

let  $\Gamma = \sqrt{(r+j\omega l)(\gamma + j\omega c)}$


$\rightarrow = \alpha + j\beta$   $\leftarrow$  propagation constant  $\frac{2\pi}{\lambda}$

attenuation  
constant

In phasor form

$$V_{\text{forward}} = V_0 e^{-\alpha z} e^{-j\beta z}$$

$V_0$  = amplitude of wave at  $z=0$

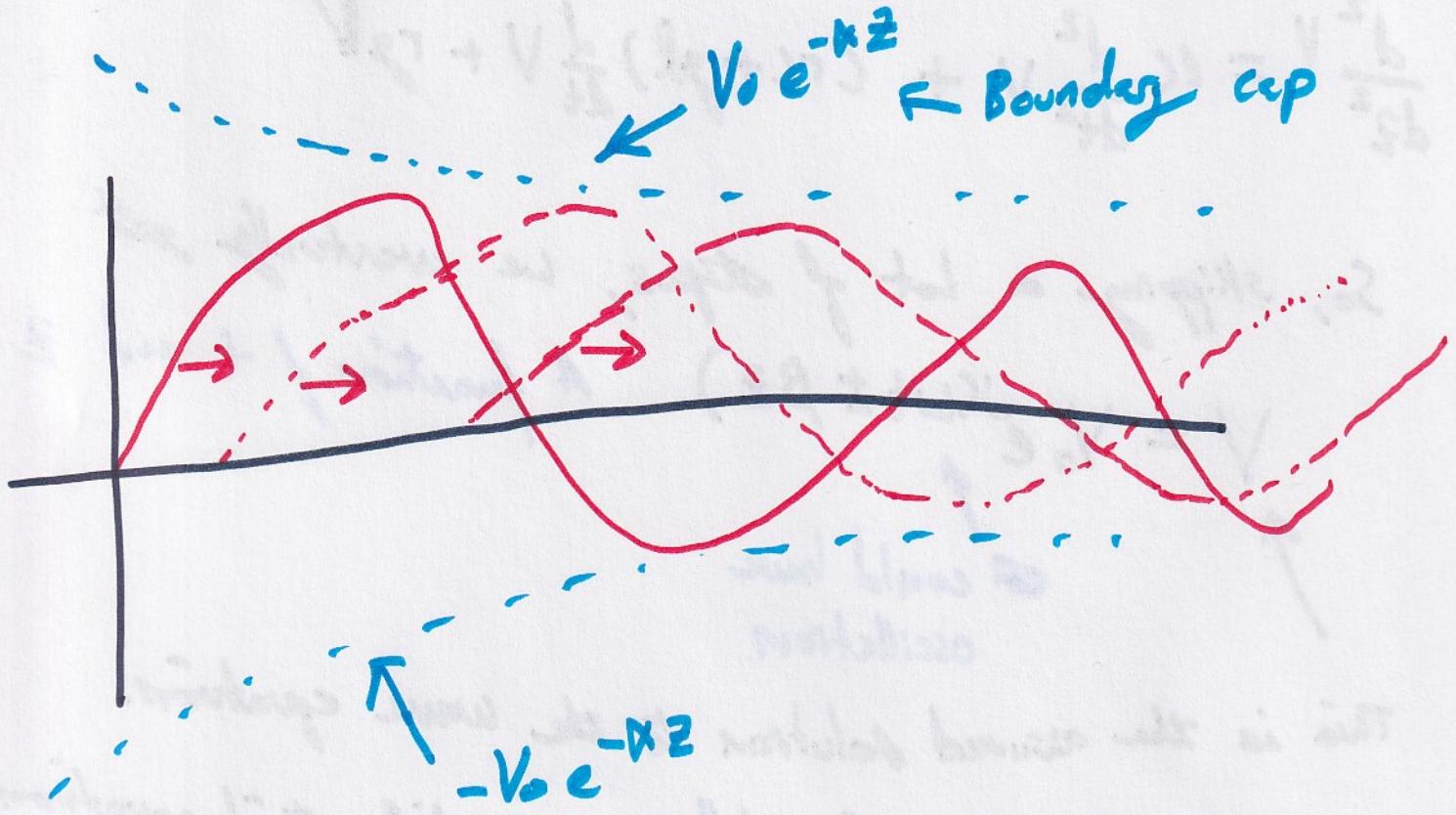

{ for the most part,  $G \rightarrow 0$  (assumed)  
and ~~R~~  $R \ll j\omega L$

we have a Low loss Line for these conditions

so as a consequence,

$$\gamma = \sqrt{(r+j\omega L)(j\omega C)} \\ \rightarrow \sqrt{(r+j\omega L)(j\omega C)}$$

After some Algebra

$$\gamma = \left( \sqrt{(j\omega C)(j\omega L)} \right) \sqrt{1 + \frac{r}{j\omega L}} \\ = \pm j\beta \left( 1 + \frac{r}{2j\omega L} \right)$$

recall  $\sqrt{1+x} \approx 1 + \frac{x}{2}$  for  $x \ll 1$

so we can write

$$\gamma = \pm j\beta \left( 1 + \frac{r}{2j\omega L} \right) = \pm (j\beta + \alpha)$$

so  $a = \frac{\beta r}{2\omega L}, V = V_0 e^{-\alpha z} e^{-j\beta z}$

10

So what does this Mean in terms of Power?

$$P = \frac{1}{2} VI^*$$

$$= \frac{1}{2} [V_0 e^{-\alpha z} e^{-j\beta z}] [I_0 e^{-\alpha z} e^{+j\beta z}]$$

$$= \frac{1}{2} V_0 I_0 e^{-2\alpha z}$$

$$= \frac{1}{2} \frac{|V_0|^2}{Z_0} e^{-2\alpha z} \quad (\text{We are ignoring the fact that } Z_0 \text{ may not be real})$$

$$= P_{\text{forward}}$$

$\rightarrow$  complex?

Lossy

$$Z_0 = \sqrt{\frac{r + j\omega L}{g + j\omega C}}$$

Lossless

$$Z_0 = \sqrt{\frac{l}{c}}$$



$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \quad \text{This is valid for low loss}$$

$$V = V_0 e^{-\alpha z} e^{-j\beta z}$$

$$P_{\text{forward}} = \frac{1}{2} \frac{|V_0|^2}{|Z_0|} e^{-2\alpha z}$$

if we say  $2\alpha z = 10$  this is long and T-line is long

do for mismatched load  
the attenuation may greatly lower the power reflected.

12

$$Z_0 = \sqrt{\frac{r+j\omega L}{j\omega C}} \quad \text{if} \quad \frac{r}{L} = \frac{j\omega}{C} \quad \text{holds}$$

$Z_0 \rightarrow \text{real}$

T-Line is lossy so  $\propto$  varies  
with freq