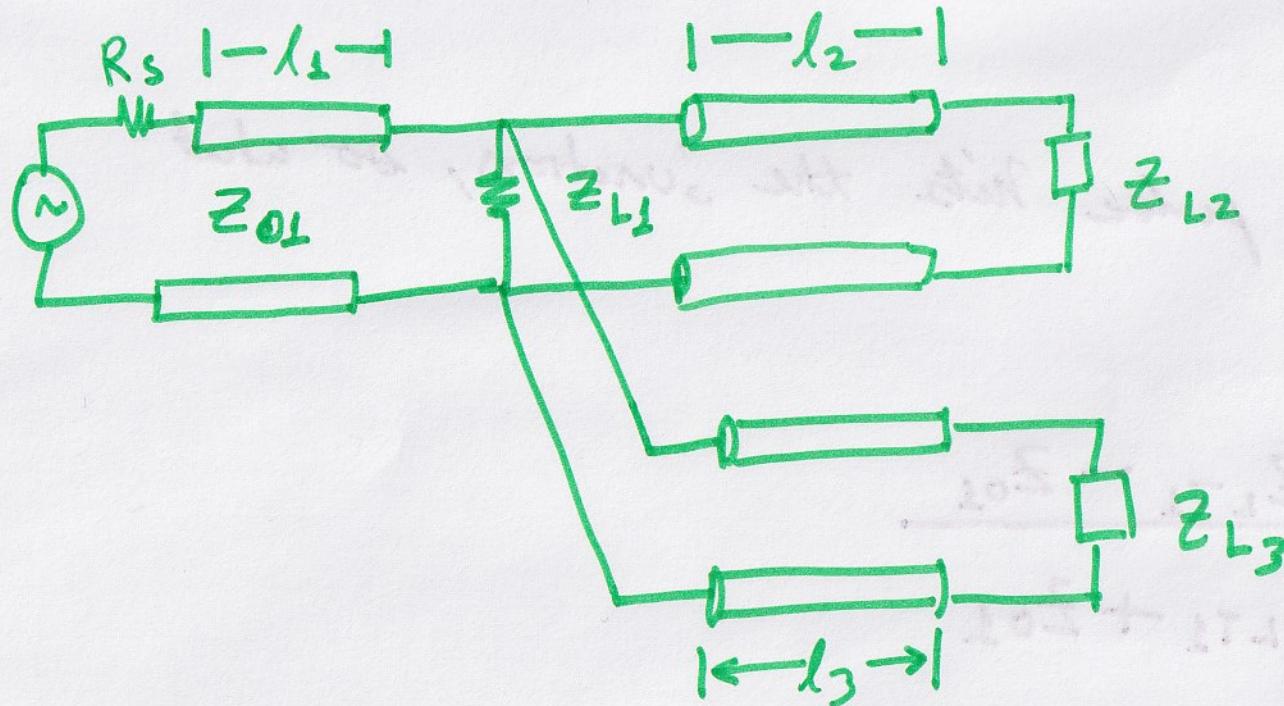


# Fields and Waves I

L 6

①



Each Line has their own time delay,  $t_d$

$$l_1 \rightarrow t_{d1} \quad (T_1)$$

$$l_2 \rightarrow t_{d2} \quad (T_2)$$

$$l_3 \rightarrow t_{d3} \quad (T_3)$$

(2)

so at  $t=0$  (No pulse yet)

$$V_o^{+} = \frac{Z_{01}}{R_s + Z_{01}} V_s$$

at  $t=t_{d1}$ , the pulse hits the junction, so what bounces back?

$$\left[ \begin{array}{l} \\ \end{array} \right] = \frac{Z_{LT1} - Z_{01}}{Z_{LT1} + Z_{01}}$$

What's  $Z_{LT1}$ ?

Since we are working with pulses, we can determine  $Z_{LT1}$  as

$$Z_{LT1} = Z_{L1} \parallel Z_{02} \parallel Z_{03} = \left( \frac{1}{Z_{L1}} + \frac{1}{Z_{03}} + \frac{1}{Z_{02}} \right)^{-1}$$

$$Z_{LT1} = \left( \frac{1}{Z_{L1}} + \frac{1}{Z_{O2}} + \frac{1}{Z_{O3}} \right) = Z_{L1} \parallel Z_{O2} \parallel Z_{O3}$$

(3)

so at  $t=t_1$ ,  $V_o^{\perp-}$  bounces back


$$V_o^{\perp-} = \boxed{LT1} V_o^{\perp+}$$

so what goes down towards  $T_2$ ?

→ A pulse, what's the amplitude?

④

## Another Problem

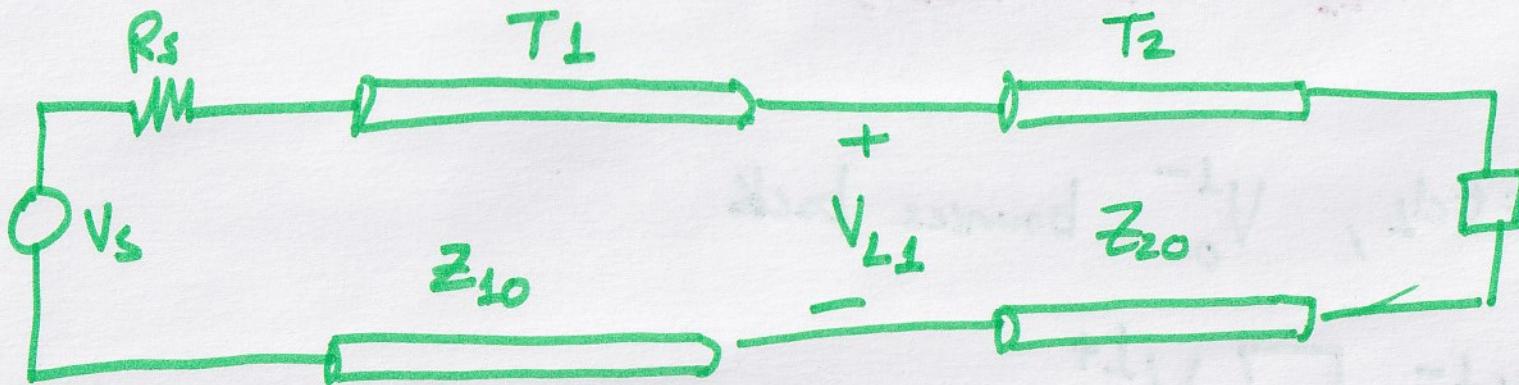

$$\text{The pulse on } T_1 \text{ is } V_1^+ = \frac{Z_{10}}{Z_{10} + R_s} V_s$$

$$\text{And the reflection coefficient for the first T-Line } (T_1) \text{ is } \Gamma_{L1} = \frac{Z_{20} - Z_{10}}{Z_{20} + Z_{10}}$$

$$\text{So } V_1^- = \Gamma_{L1} V_1^+$$

$$\text{We may write } V_{L1} = (1 + \Gamma_{L1}) V_1^+$$

What's the voltage on  $T_2$ ? (The transmitted Voltage) (5)

We know  $T_2$  is the Load for  $T_1$  and the Load for  $V_{L1}$ .

$$\text{So } V_2^+ = (1 + \Gamma_1) V_1^+$$

↑  
This is the pulse sent down  $T_2$

Power doesn't increase

Looking at the reflection coefficient,  $\frac{Z_L - Z_0}{Z_L + Z_0}$ ,  $Z_L$  must be larger for increased voltage

⑥

$$\text{so } \frac{V_L}{Z_L} = I \quad , \text{ if } Z_L \uparrow , I \downarrow$$

then Power doesn't go up.

Therefore, going back to the previous problem, the amplitude of the pulse being sent down  $T_2$  and  $T_3$  is

$$V_0^{2,3+} = (1 + \frac{1}{L_{T_1}}) V_0^{1+}$$


# AC Steady State Impedance Matching

7

Ideally, we want  $\Gamma_L = 0$

which means we have no reflected power

Example)

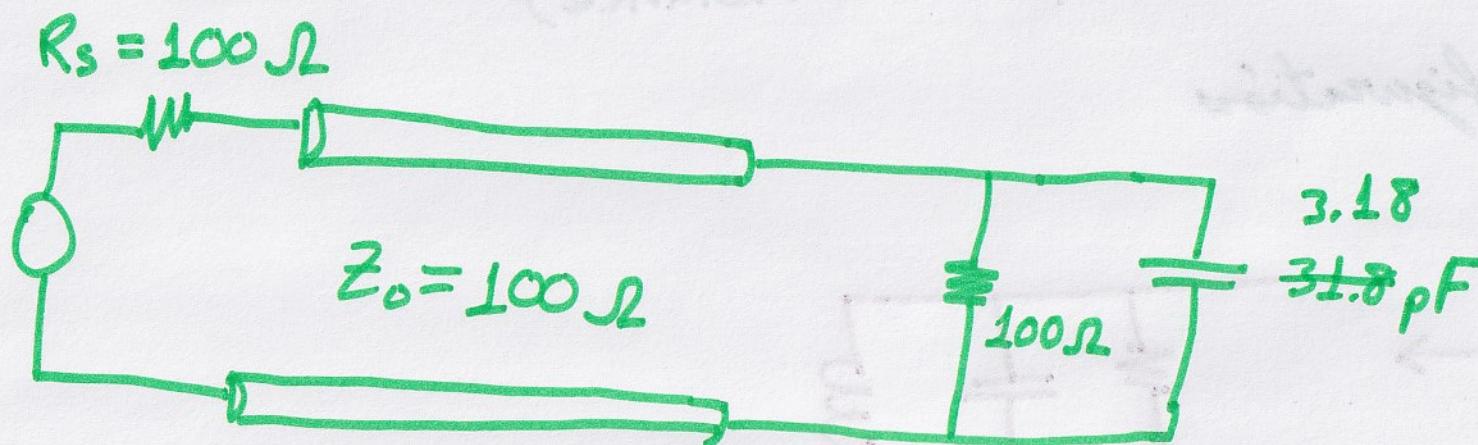

$V_s$  at 100V at 1MHz

(8)


We can see we have a mismatched Load

$$Z_L = R \parallel \frac{-j}{\omega C} = 100 \parallel -j50$$

The goal is to reduce the capacitive reactance to zero  
(negative reactance)

We do this by adding inductive reactance in parallel  
(positive reactance)

for this configuration

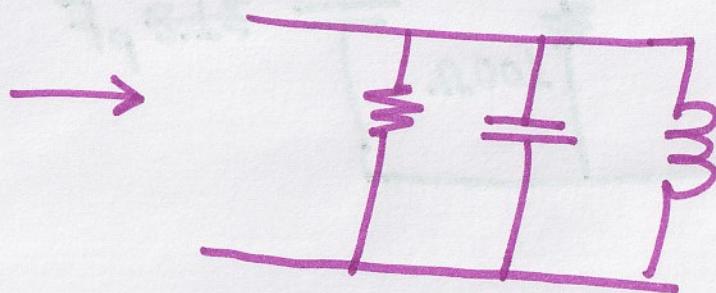

$$\text{if } |Z_L| = |Z_C|, \text{ Then } Z_L = Z_C^*$$
(9)

equal and opposite

So we need

$$Y_{\text{Load}} = Y_R + Y_L + Y_C$$

effective admittance (Load)      These need to cancel out


$$\rightarrow Y_{\text{Load}} = Y_R \quad (Z_L = R)$$

effective impedance (Load)

When you change the frequency, the reactance of the capacitance and inductance change. So to keep a matched Load we have to design around a given frequency ( $\omega$ )

(10)

Here's what we can do

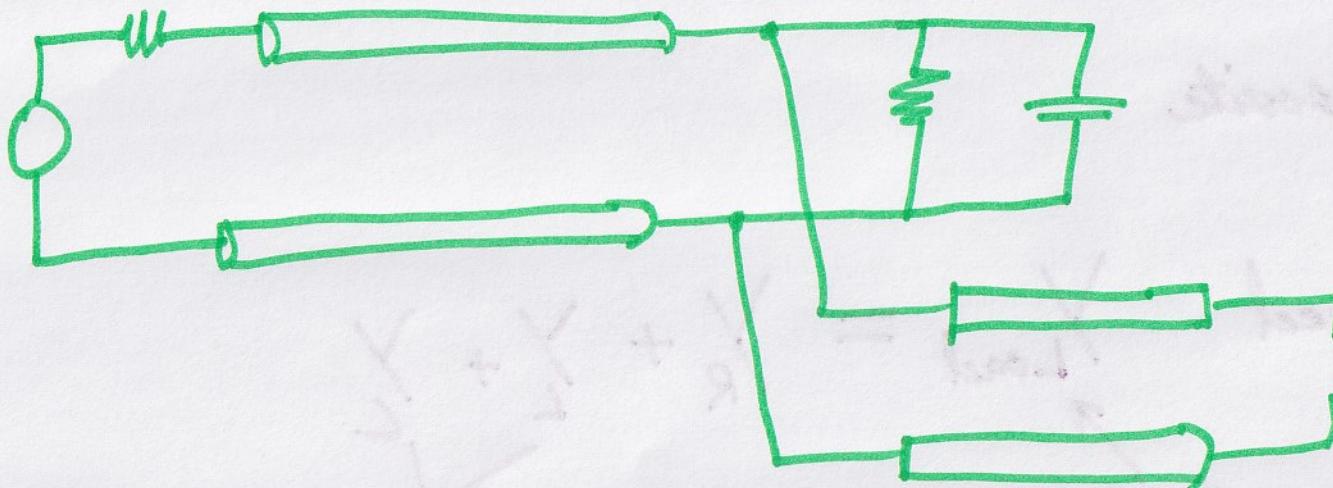

add an open circuit

$$\rightarrow Z_{inoc} = Z_0 \left( \frac{\infty + jZ_0 \tan \beta l}{Z_0 + j\infty \tan \beta l} \right)$$

$Z_{inoc}$   
( $Z$  input open  
circuit)

$$= Z_0 \left( \frac{\infty}{j\infty + \tan \beta l} \right)$$

$$= -j Z_0 \frac{1}{\tan \beta l}$$


so our effective load

$$Z_{L(\text{effective})} = 100 \parallel -j50 \parallel \frac{-jZ_0}{\tan\beta L}$$

↓                   ↑                   ↑  
 Resistor          Capacitor          Open circuit stub

We want  $Z_{L(\text{effective})} = 100$

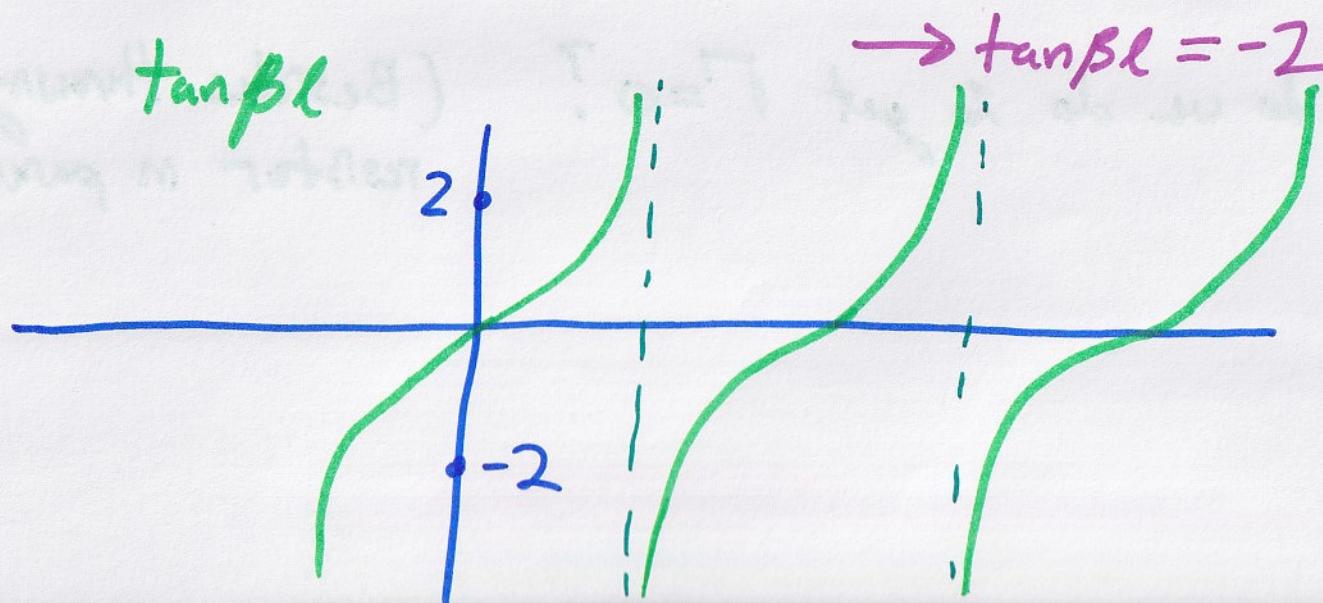
Stub works if  $Z_{in,oc} = +j50 \rightarrow j50 = \frac{-jZ_0}{\tan\beta L} \quad (Z_0 = 100 \Omega)$



(12) Find an answer that corresponds to '-2'

The shortest Line is desired so we don't have  
so much Loss of Power

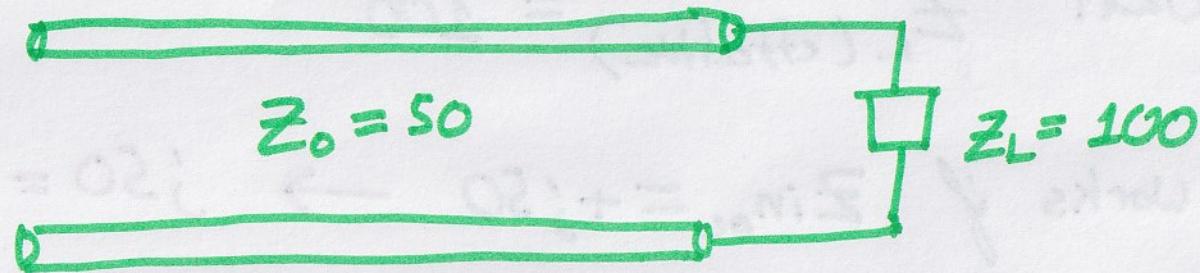
Example) What if we have a mismatched resistive Load



What do we do to get  $\Gamma=0$ ? (Besides throwing a 100Ω resistor in parallel)

We can put another Transmission Line  $m$  between the Original Transmission Line and the  $100 \Omega$  Load.

(13)

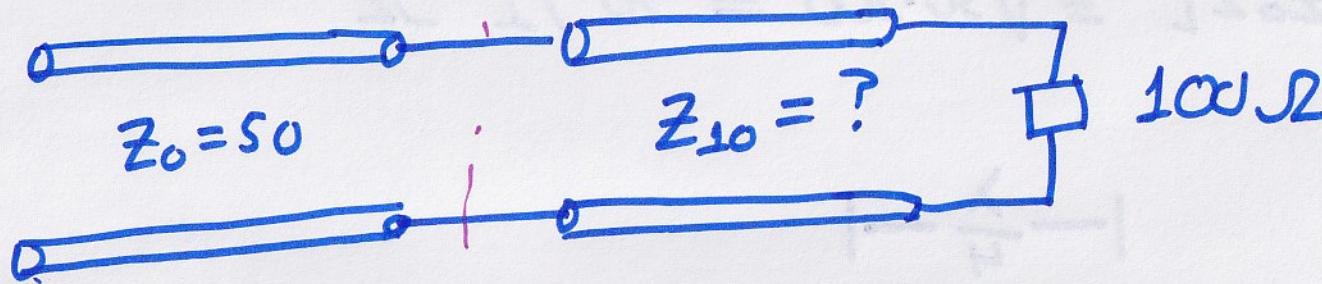

$\rightarrow Z_{in} = 50 \Omega$  we need  $50 \Omega$  to get a matched Load

$$Z_{in} = Z_{10} \frac{Z_L + jZ_{10} \tan(\beta l)}{Z_{10} + jZ_L \tan(\beta l)}$$

We can manipulate  $Z_{in}$  by adjusting the Length of the second Transmission Line.

$$l = \frac{\lambda}{2} \rightarrow Z_{in} = Z_L$$

$$l = \frac{\lambda}{4} \rightarrow Z_{in} = \frac{Z_{10}^2}{Z_L}$$


(14)

We want

$$Z_{in} = Z_0 = \frac{Z_{10}}{Z_L}$$

$$Z_{10} = \sqrt{Z_0 Z_L} = \sqrt{50 \cdot 100} = 70.71 \Omega$$

So then

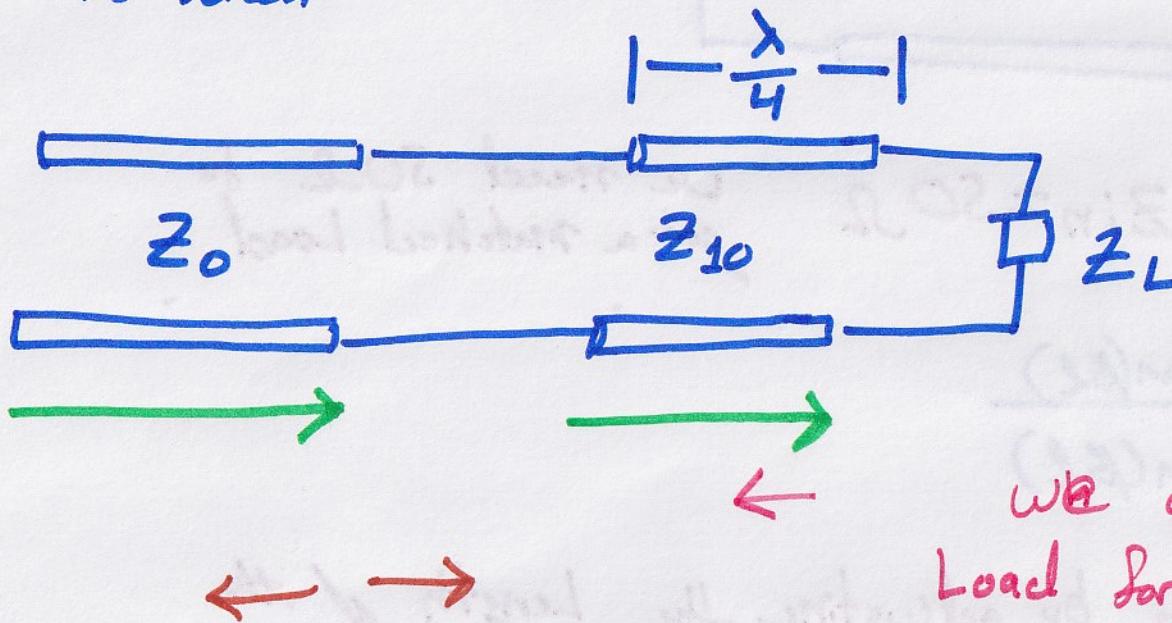


We don't have a matched load for the second transmission line. So there is a reflected wave.

And  $T_2$  (second T-line) sees a reflection coefficient due to  $T_1$  (first T-line),  ~~$Z_{inT_2}$~~   $\rightarrow \frac{Z_{inT_1} - Z_{10}}{Z_{inT_1} + Z_{10}}$

~~where~~  $\Rightarrow$


where  $Z_{inT1} = Z_0 \frac{R_s + jZ_0 \tan \beta L}{Z_0 + jR_s \tan \beta L}$

(15)

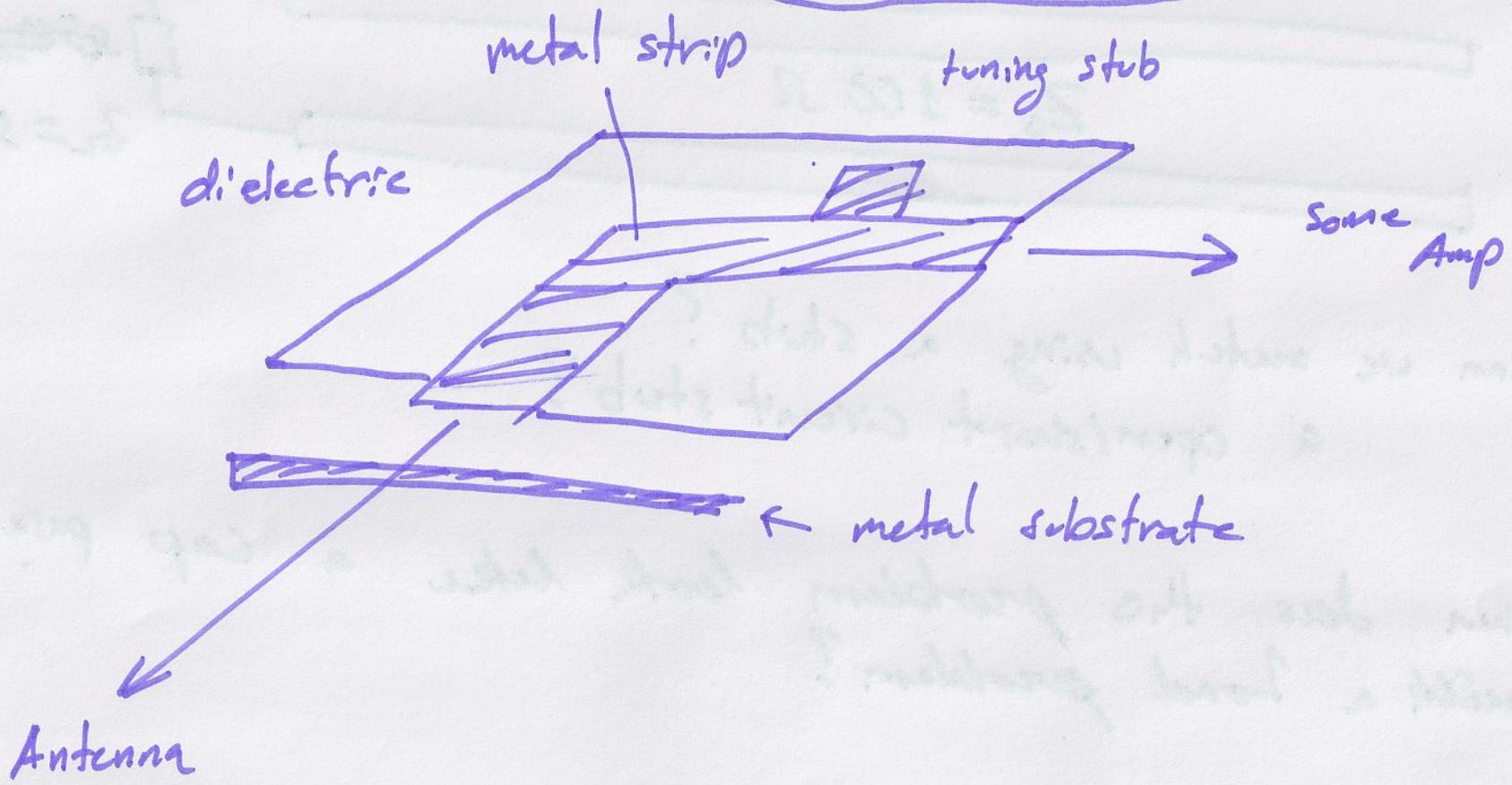

(16)

Ex)

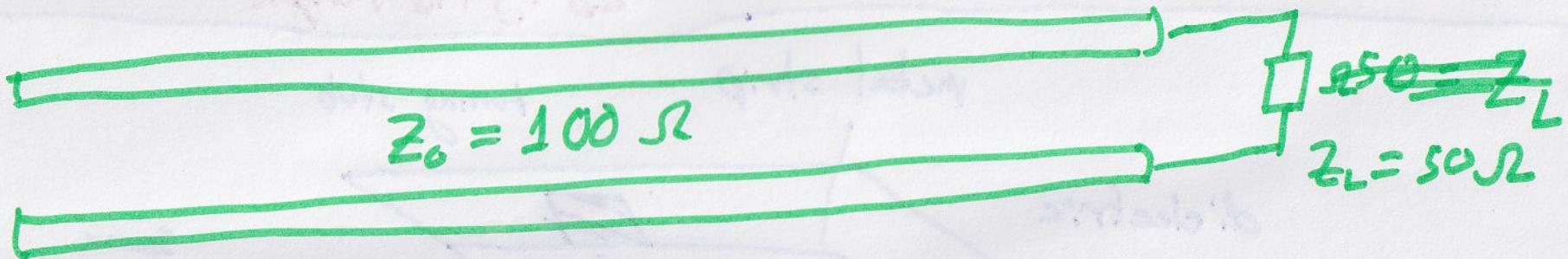

Can we match using a stub?  
a open/court circuit stub?

When does this problem look like a cap parallel  
with a load problem?

Think about  $Z_{in}$

$$Z_{in} = Z_0 \frac{Z_L + j Z_0 \tan(\beta l)}{Z_0 + j Z_L \tan(\beta l)}$$



at  $\ell = 0, \frac{\lambda}{2}, \frac{\lambda}{4}, \frac{3}{2}\lambda$

$$\rightarrow Z_{in} = 50 \Omega$$


at  $\ell = \frac{\lambda}{4}, \frac{3}{4}\lambda, \frac{5}{4}\lambda$

$$\rightarrow Z_{in} = \frac{z_0^2}{z_L} = 200$$

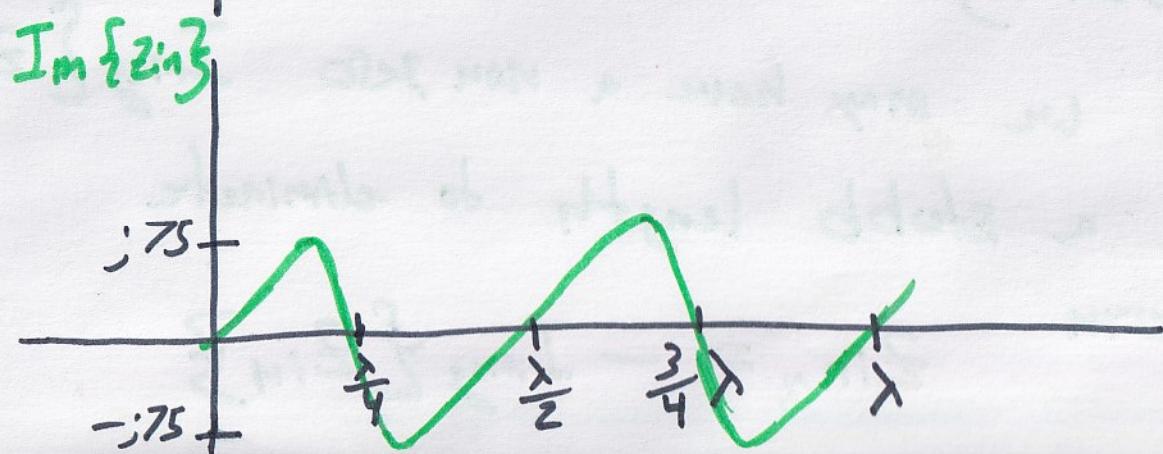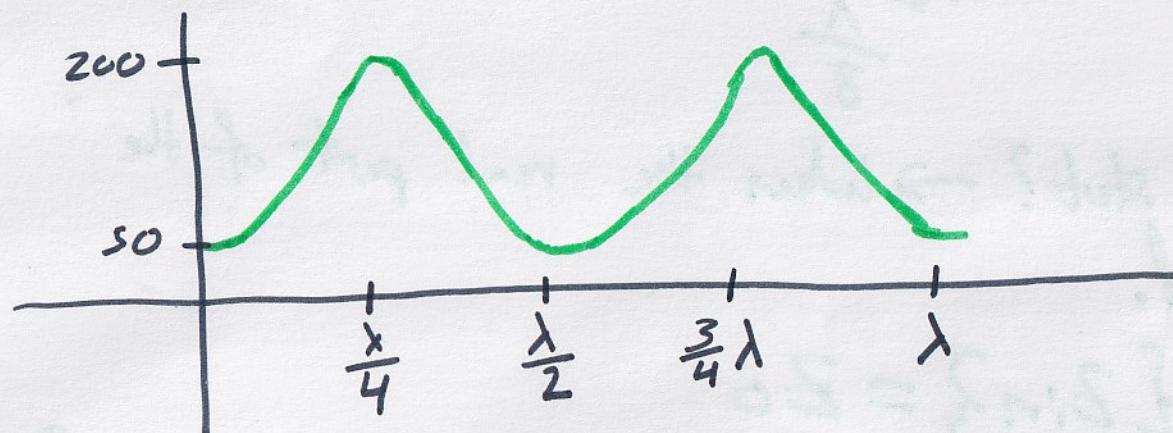$Re\{Z_{in}\}$   $50 < Re\{Z_{in}\} < 200$



(18)

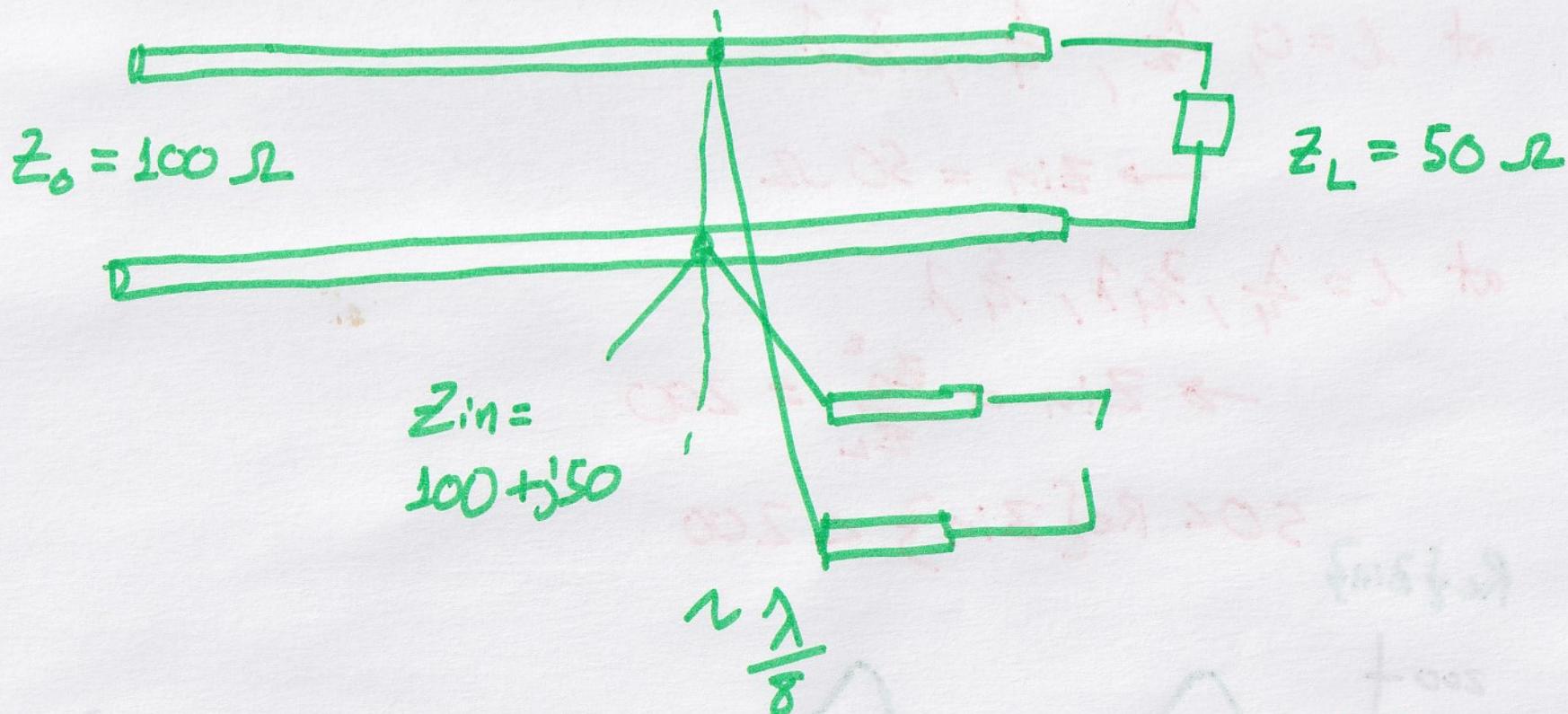

Where do we put this stub?  $\rightarrow$  When the real part of the Impedance is matched.

$$\operatorname{Re}\{Z_{in}\} = Z_0$$


But at this point, we may have a non zero  $\operatorname{Imag}\{Z_{in}\}$   
 $\rightarrow$  So use a stub length to eliminate this term

$$Z_{in\alpha} = -\operatorname{Imag}\{Z_{in}\}$$

# Double stub tuning

(19)

(open/short  
ckt)

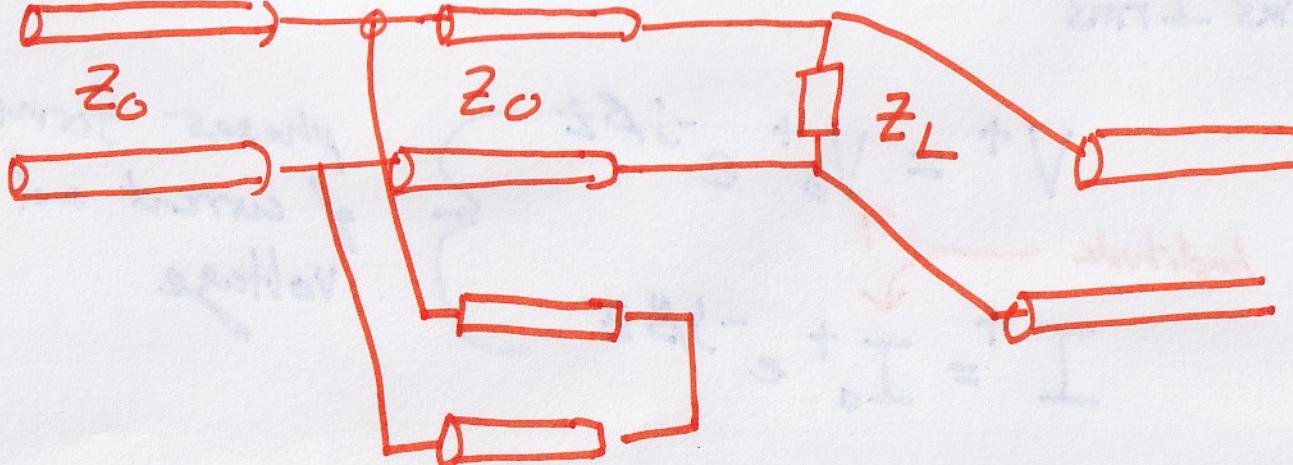

Use Smith charts!

(20) Power =  $\frac{1}{2} VI^*$  ← complex conjugate of  $I$   
 $= V_{rms} I_{rms}^*$

~~$V_o^+ = Z_o^+$~~

~~$I_o^+ = Z_o^+$~~

$V^+ = V_o^+ e^{-j\beta z}$

$I^+ = I_o^+ e^{-j\beta z}$

Amplitude

} phases form  
of current and  
voltage

Power =  $\frac{1}{2} (V_o^+ e^{-j\beta z}) \left( \frac{V_o^+}{Z_o} e^{-j\beta z} \right)^*$   
 $= \frac{1}{2} (V_o^+ e^{-j\beta z}) \left( \frac{V_o^+}{Z_o} e^{+j\beta z} \right)$

Power =  $\frac{1}{2} \frac{|V_o^+|^2}{Z_o}$

This is the Power of the  
forward propagating wave

E1

Reflected Wave

$$V^- = V_{OR}^- e^{+j\beta z}$$

$$I^- = I_{OR}^- e^{+j\beta z} = \frac{V_{OR}^-}{Z_0} e^{+j\beta z}$$

$$\rho_{\text{reflected}} = \frac{1}{2} \frac{|V_{OR}|^2}{Z_0} \quad V_{OR} = \Gamma V_{0f}$$

$$= \frac{1}{2} \left| \frac{\Gamma V_0}{Z_0} \right|^2 = |\Gamma|^2 \left( \frac{1}{2} \frac{|V_0|^2}{Z_0} \right)$$

 $s_0$ 

$$\rho_{\text{reflected}} = |\Gamma|^2 P_{\text{forward}}$$

reflected power is proportional to  $|\Gamma|^2$

(22)


Ex) if  $\Gamma = \frac{1}{3}$ ,  $\frac{1}{3}$  Voltage is reflected  
but  $\frac{1}{9}$  Power is reflected.

Power delivered to the Load is the Power transmitted?  
(Same question)

---

$$P_{\text{Load}} = (1 - |\Gamma_L|^2) P_{\text{Forward}}$$

Look at Source resistance.

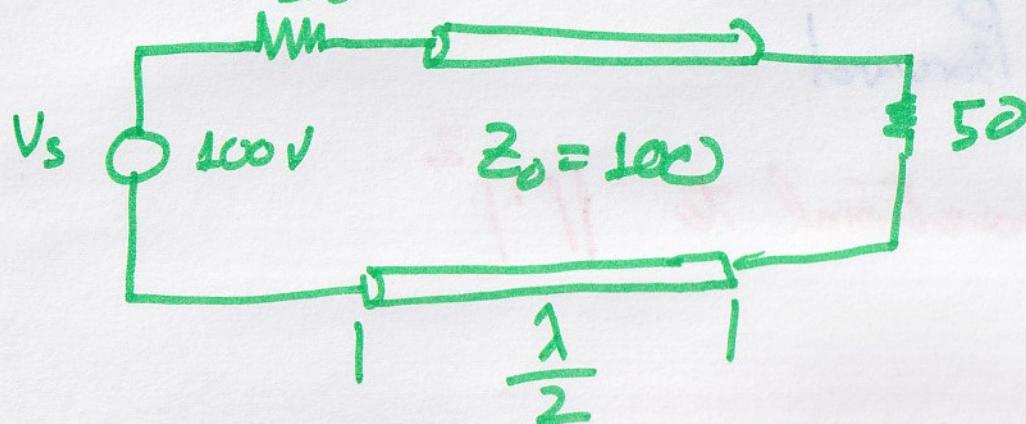


What's the forward Power?

(23)

~~By AC~~ if  $\ell = \frac{\lambda}{2}$ ,  $Z:n = 50$

equivalent ckt

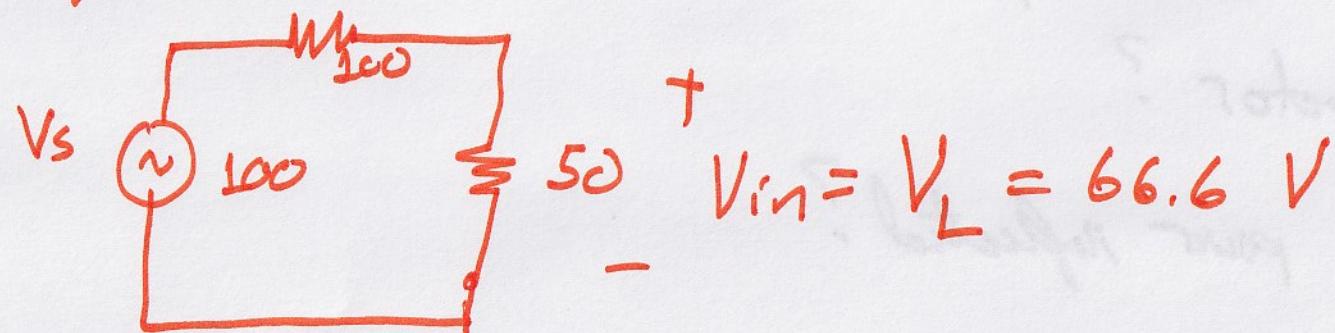

$$P_L = \frac{1}{2} \frac{(66.67)^2}{50} = 44.4 \text{ [W]}$$

$$\begin{aligned} \text{So Then } P_L &= (1 - |\Gamma|^2) P_{\text{forward}} \\ &= (1 - (\frac{1}{3})^2) P_{\text{forward}} \end{aligned}$$

$$\rightarrow P_{\text{forward}} = \frac{44.4}{8/9} = 49 \text{ W}$$

(24)

So we have about 90% efficiency

What about a Capacitive Load?  
or Inductors?

All power reflected?



$$[4] \quad \eta_{pp} = \frac{P_{pp}}{P_{in}} = 90\%$$

$$\begin{cases} C(\tau) - 1 = 0 & \text{left} \\ C(\tau) - 1 = 1 & \text{right} \end{cases}$$

$$\eta_{pp} = \frac{P_{pp}}{P_{in}} = 90\%$$