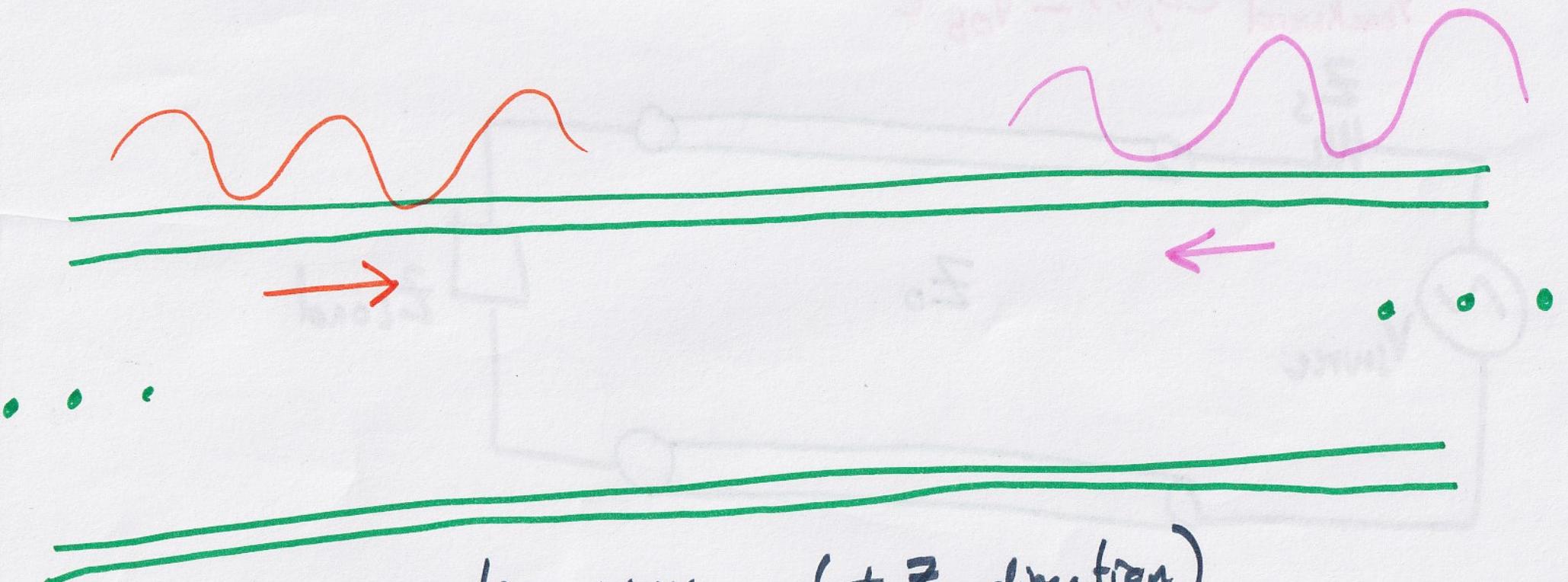


# Fields and Waves I

L3



The Reflection Coefficient




Forward propagating wave (+z direction)

$$V_{\text{forward}}(z, t) = V_0 e^{j(\omega t - \beta z)}$$

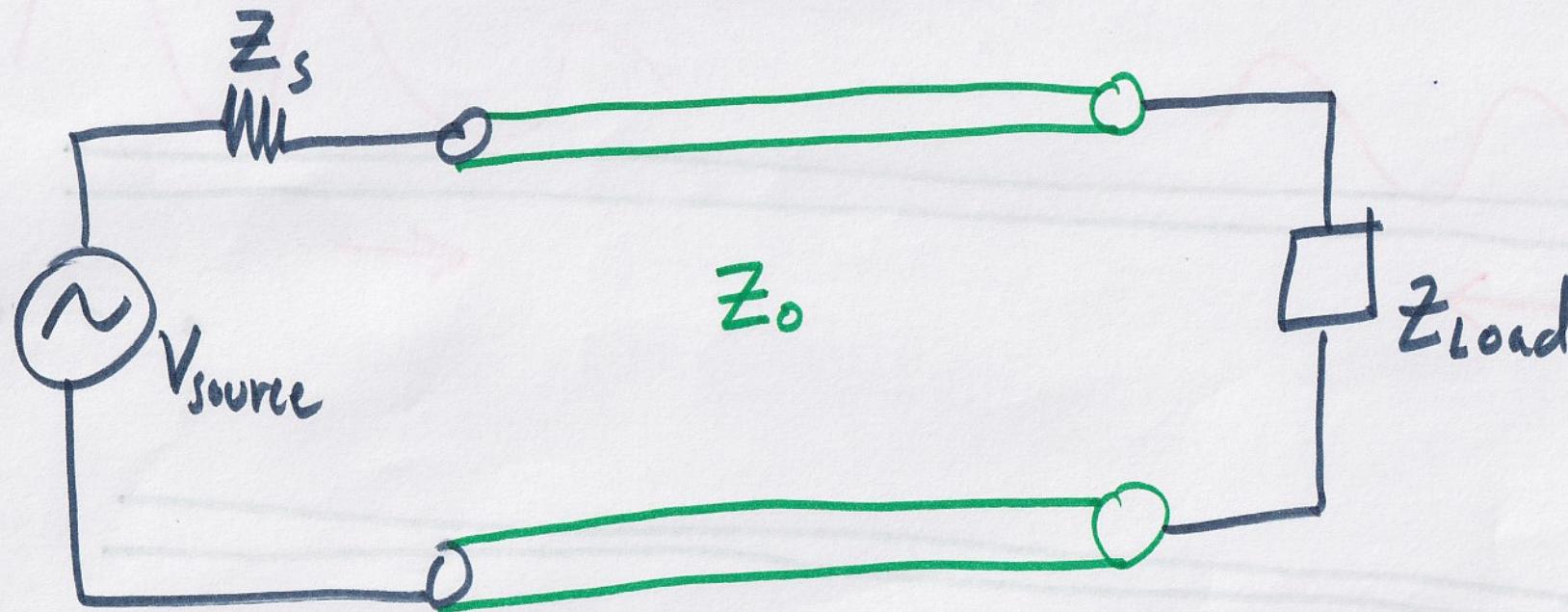(2) backward propagating wave (-z direction)

$$V_{\text{backward}}(z, t) = V_0 e^{j(\omega t + \beta z)}$$



burr

ckt

(3)

$Z_s \rightarrow$  Source impedance if resistive,  
 $Z_L \rightarrow$  load impedance They dissipate power

$Z_0 \rightarrow$  characteristic impedance of T-line  
if real, Line itself is lossless

$Z_0$  is not a resistor, just a line of  
Transmission just

if DC, the ckt is a voltage divider

(4)

"Think" waves in a bathtub reflect backwards

Note, we ~~are~~ <sup>are</sup> dealing with phasors

$$V_{df} = V_0 e^{j(\omega t - B z)} \longleftrightarrow V_0 e^{-j B z}$$

phasor

So then,

Forward propagating waves come from the source

Backward propagating waves come from the  
Load  $\rightarrow$  reflected waves

Denote Blue as

$$V_{\text{forward}} = V_{\text{of}} e^{-jBz}$$

Denote Red as


$$V_{\text{reflected}} = V_{\text{ob}} e^{+jBz}$$

From now on, we'll stick to this definition for the remainder of Transmission Lines

(6)

Assign an origin for coordinate system

(it's just a reference)

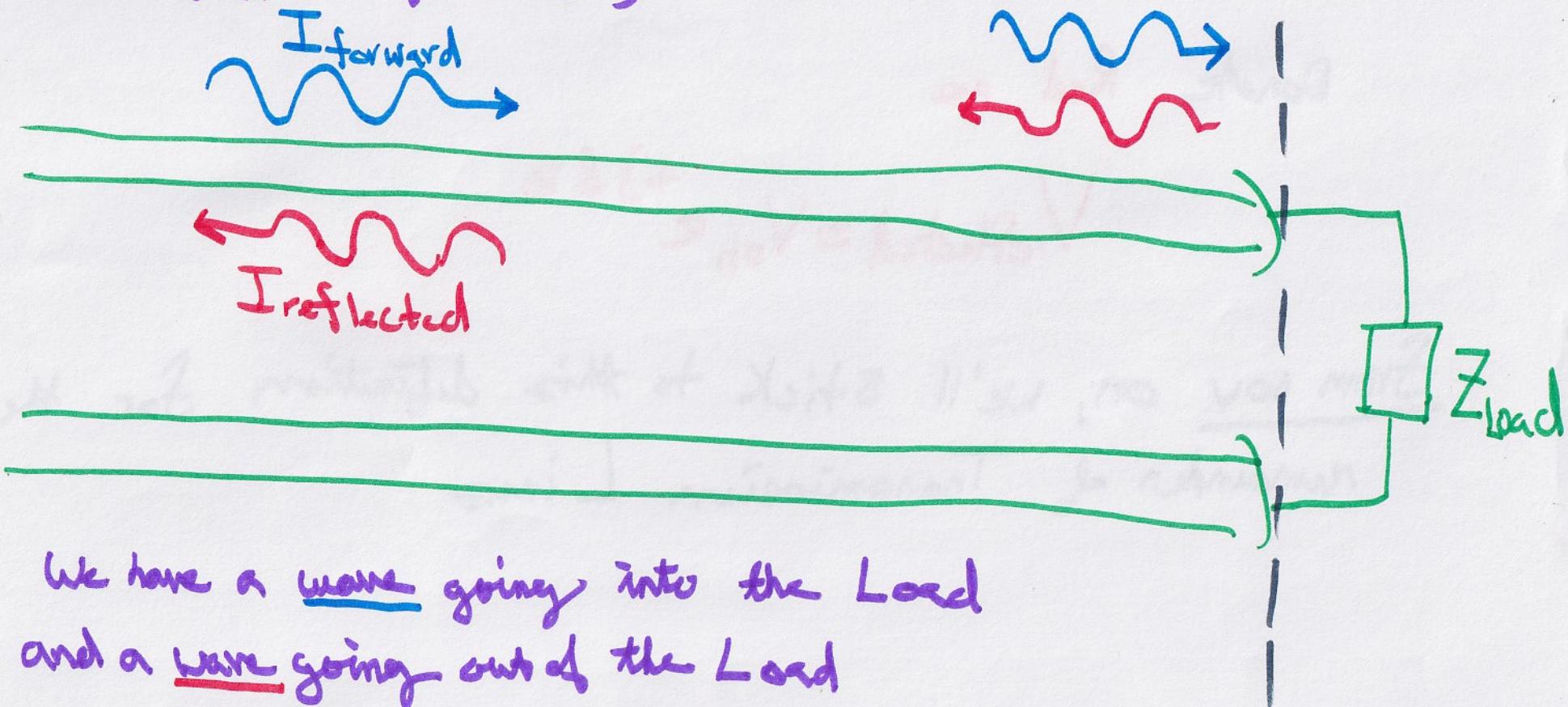

We have a wave going into the Load  
and a wave going out of the Load

The Waves just add

$Z=0$   
(position)

$$V_{\text{total}} = \underline{V_{\text{forward}}} + \underline{V_{\text{reflected}}}$$

(7)

$$V_{\text{total}} = V_{\text{of}} e^{-j\beta z} + V_{\text{or}} e^{+j\beta z}$$

$z$  = position    $\beta$  is constant (constant)

$$V_{\text{total}}(z=0) = V_{\text{of}} + V_{\text{or}} = V_{\text{load}}$$

$z=0$ , means or are at the Load

$$V_{\text{total}}(z=0) = V_{\text{of}} e^{-j\beta z} + V_{\text{or}} e^{+j\beta z} = V_{\text{load}}$$

for now, let's say this is partially true

(8)

So

$V_{os}$  is known via source constraint

$V_{or}$ , unknown

$V_{load}$ , unknown

(2) unknowns

1 equation so far

$$I_{\text{forward}} = I_{of} e^{-jBz}$$

$$I_{\text{backward}} = I_{or} e^{+jBz}$$

(reflected)

$$I_{\text{forward}} = \frac{V_{of}}{Z_0} e^{-jBz}$$

$$I_{\text{reflected}} = \frac{V_{or}}{Z_0} e^{+jBz}$$

Question!

So do I current waves add?

No! current waves subtract

(9)

$$I_{\text{total}} = I_{\text{forward}} - I_{\text{reflected}}$$

$$= \frac{V_{0f}}{Z_0} e^{-jBz} - \frac{V_{0r}}{Z_0} e^{+jBz}$$

At  $z=0$  (The Load)

$$I_{\text{total}} = \frac{V_{0f}}{Z_0} - \frac{V_{0r}}{Z_0} = I_{\text{Load}} = \frac{V_{\text{load}}}{Z_{\text{load}}}$$

we can do this by KCL

→ This is our 2nd equation

(10)

$$V_{os} + V_{or} = V_{load}$$

2 equations

$$\frac{V_{os}}{Z_0} - \frac{V_{or}}{Z_0} = \frac{V_{load}}{Z_{load}}$$

2 unknowns

→ we know  $V_{os}$ 

So, we have a relation

After a bunch of Algebra,

$$V_{reflected} = \boxed{V_{os forward}}$$

↑  
reflection coefficient

We may write

$$V_{0f} \left( \frac{1 + \Gamma}{Z_0} \right) = V_{load}$$

$$\boxed{V_{0f} = \Gamma V_{0f}}$$

$$V_{0f} \left( \frac{1 - \Gamma}{Z_0} \right) = \frac{V_{load}}{Z_{load}}$$

Solve for  $\Gamma$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$V_{total} = V_o [e^{-j\beta z} + \Gamma e^{+j\beta z}] \{ e^{+j\omega t} \}$$

$$I_{total} = \frac{V_o}{Z_0} [e^{-j\beta z} - \Gamma e^{+j\beta z}] \quad \text{"implied"}$$

(12)

So what if  $\Gamma = 0$ ?

→ Nothing is reflected

---

We don't want waves reflected

Now we ask ourselves, is this ~~always~~ possible?  
always

Short Circuit

$$Z_L = 0$$

$$\Gamma = \frac{0 - Z_0}{0 + Z_0} = -1$$

What does this mean?

---

for  $\Gamma = -1$

$$V_{or} = (-) V_{os} \rightarrow |V_{or}| = |V_{os}|$$

Here's a consequence,

if  $z_L = 0$ , power to the Load is entirely reflected. (Which is bad)

What's the voltage at the Load?

$$V_{total} = V_0 [e^{-jBz} + \Gamma e^{+jBz}] \Big|_{z=0}$$

$$= V_0 [1 + \Gamma]$$

$$= 0 \quad \text{when } \Gamma = -1$$

⑯

What's the current at the Load?

$$I_{\text{total}} = \frac{V_0}{Z_0} [e^{-j\beta z} - \Gamma e^{+j\beta z}] \Big|_{z=0}$$

$$= \frac{V_0}{Z_0} [1 - \Gamma]$$

For a short circuit ( $Z_L = 0$ )

$$\Gamma = -1 \quad I_{\text{total}}(z=0) = \frac{V_0}{Z_0} (2)$$

$\Rightarrow$  The current waves are adding constructive interference

But twice the current isn't useful without power

What about an open circuit?

(15)

$$Z_L \rightarrow \infty, \quad \Gamma = \frac{\infty - Z_0}{\infty + Z_0} \rightarrow 1$$

So for  $\Gamma = 1$


$$\left. \begin{array}{l} V_{\text{Load}} = 2V_0 \\ I_{\text{Load}} = 0 \end{array} \right\} \quad \underbrace{P_{\text{Load}} = 0}_{(\text{We are now using } V_{0f} = V_0)}$$

And for short circuit

$$\left. \begin{array}{l} V_{\text{Load}} = 0 \\ I_{\text{total}} = \frac{V_0}{Z_0} (2) \end{array} \right\} \quad P_{\text{Load}} = 0$$

16

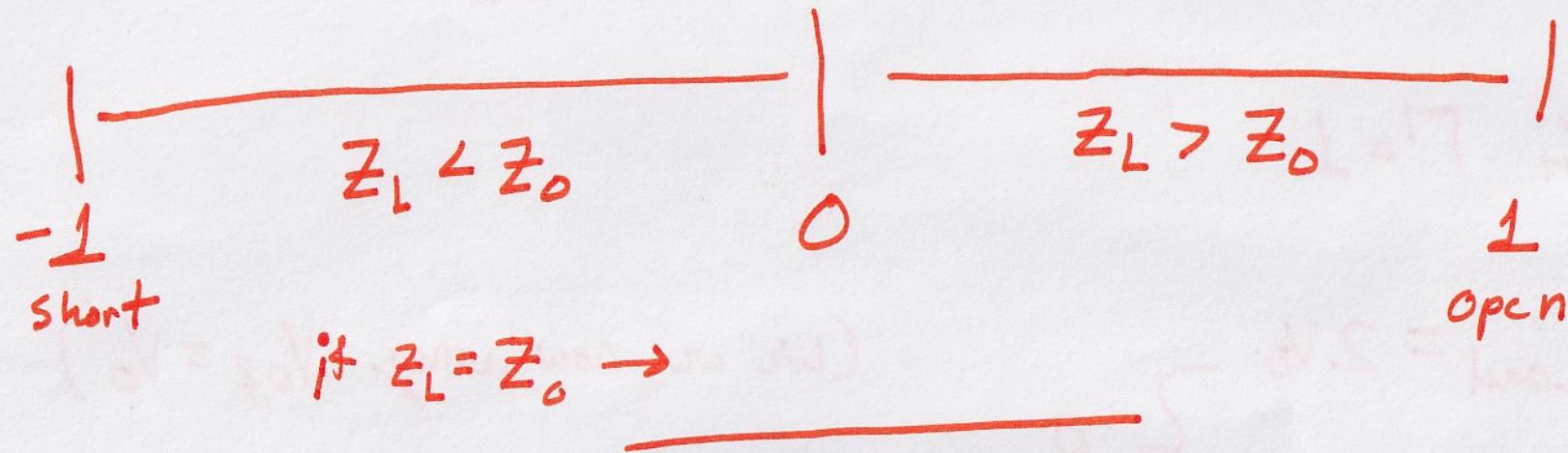For resistive Loads  $\rightarrow \Gamma_{\text{real}} -1 < \Gamma < 1$



Note, Amplitude of reflected wave does not exceed the wave from the source

for  $-1 < \Gamma < 1$

Amplitude of reflected wave  $\leq$  Amplitude of forward wave

# Let's Look at Power

17

$$\text{Let } Z_0 = 100 \Omega$$

$$Z_L = 50 \Omega$$

$$\text{so } \Gamma = \frac{50 - 100}{50 + 100} = -\frac{1}{3} \quad \Gamma \text{ is now negative}$$

$$V_{\text{total}} = 10(e^{-jBz} - \frac{1}{3}e^{+jBz})$$

$$V_{\text{Load}}(z=0) = 10 \left( 1 - \frac{1}{3} \right) = 6.66 \text{ V}$$

Voltage Amplitude

$$\Rightarrow V_{\text{load}} = 6.66 \cos(\omega t)$$

remember, this is the phasor form, we don't see the  $e^{j\omega t}$ . And the measurable wave is a cosine

18) Recall ohm's Law, calculate Power

$$P = \frac{V^2}{Z_L} = \frac{(6.66)^2}{50} \approx \frac{400}{450} [W]$$

(Let's call it rms to make us happy)

Another Example

(19)


$$Z_0 = 100 \Omega \quad Z_L = 200 \Omega, \quad \Gamma = \frac{200 - 100}{200 + 100} = \frac{1}{3}$$

$$V_{\text{Load}} = 10 \left(1 + \frac{1}{3}\right) = \frac{40}{3} = 13.33 V$$

$$P = \frac{V^2}{Z_L} = \frac{\left(\frac{40}{3}\right)^2}{200} \approx \frac{400}{450} [W]$$

(20)

Look at the T-Line now

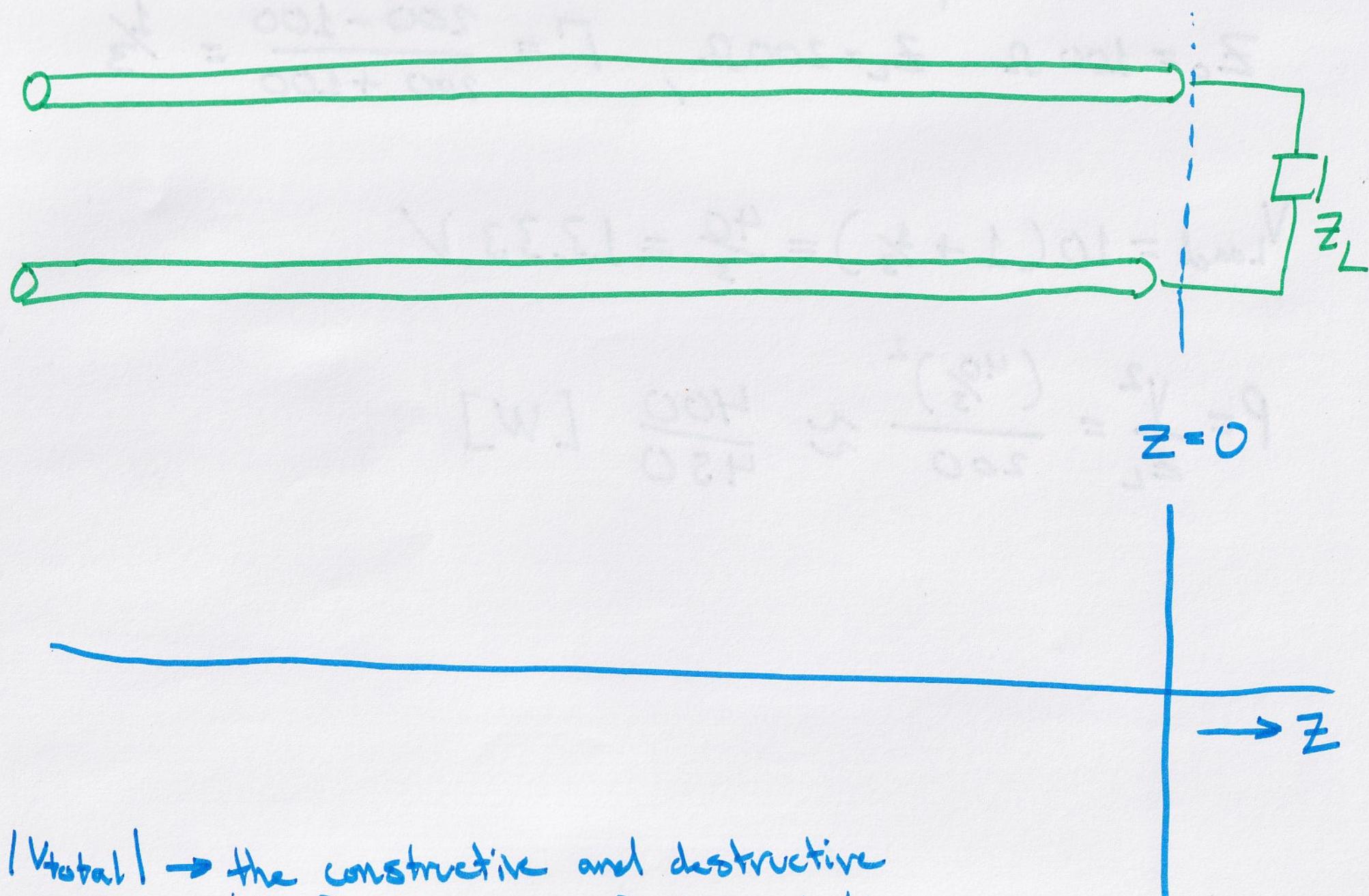

$|V_{\text{total}}| \rightarrow$  the constructive and destructive interference as a function of time

so we can write

$$|V_{\text{total}}| = |V_0(e^{-jBz} + \Gamma e^{+jBz})| \\ = |V_0| |(1 + \Gamma e^{+2jBz})| |e^{-jBz}|$$

we know  $|e^{-jBz}| = 1$

because,  $|e^{j\phi}| = |\cos(\phi) + j\sin(\phi)| \\ = (\cos^2(\phi) + \sin^2(\phi))^{1/2} = 1$

so  $|V_{\text{total}}| = |V_0| |(1 + \Gamma e^{+2jBz})|$


(22)

Ex)

$$Z_L = 100 \Omega \quad Z_0 = 100 \Omega$$

$$\Rightarrow \boxed{\Gamma = 0}$$

so  $|V_{\text{total}}(Z)| = |V_0|$

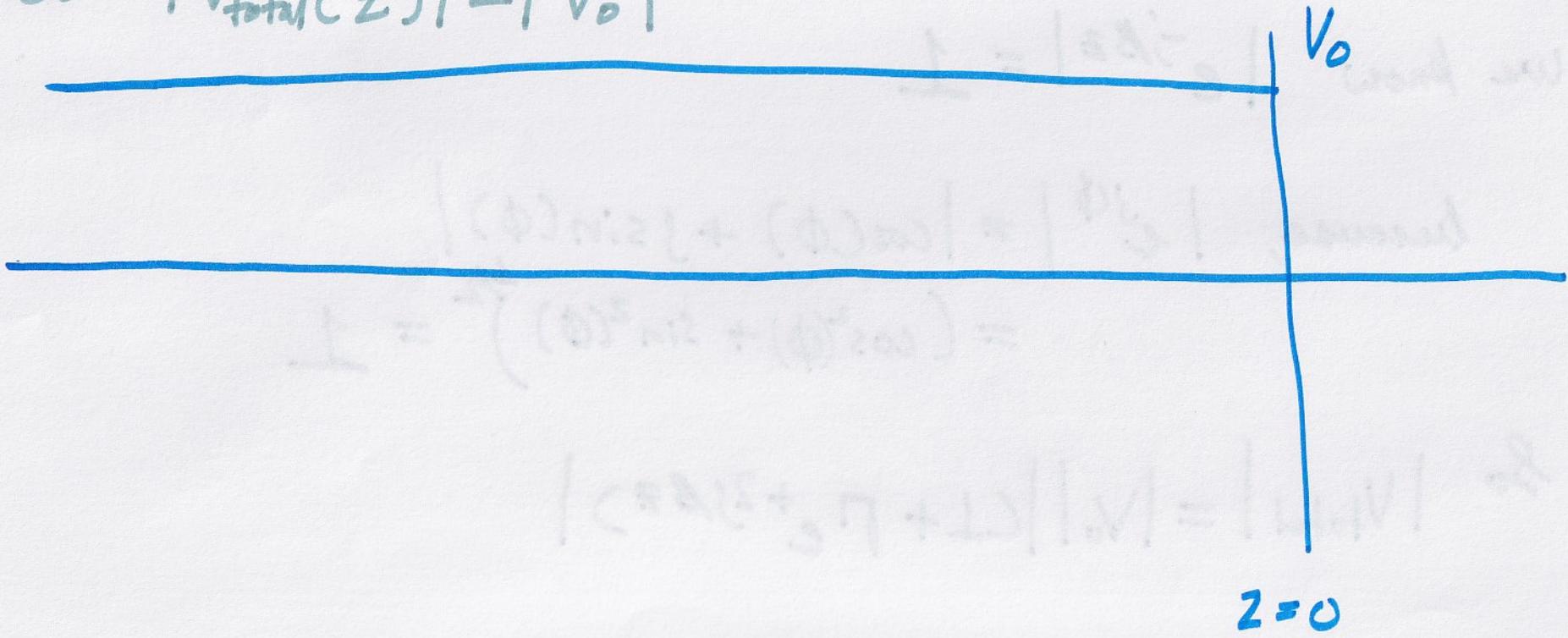

So, what does this mean?

$|V_{\text{total}}(z)|$  is amplitude as a function of position

(23)

$|V_{\text{total}}(z)|$  is measured everywhere at the T-line

This is not a ~~sinusoid~~


sinusoid as  $|V_0|$  is amplitude

In general,  $V_{\text{total}}$  is a "standing wave pattern"


(24)

blue is forward, red is reflected


$V_{\text{total}}$

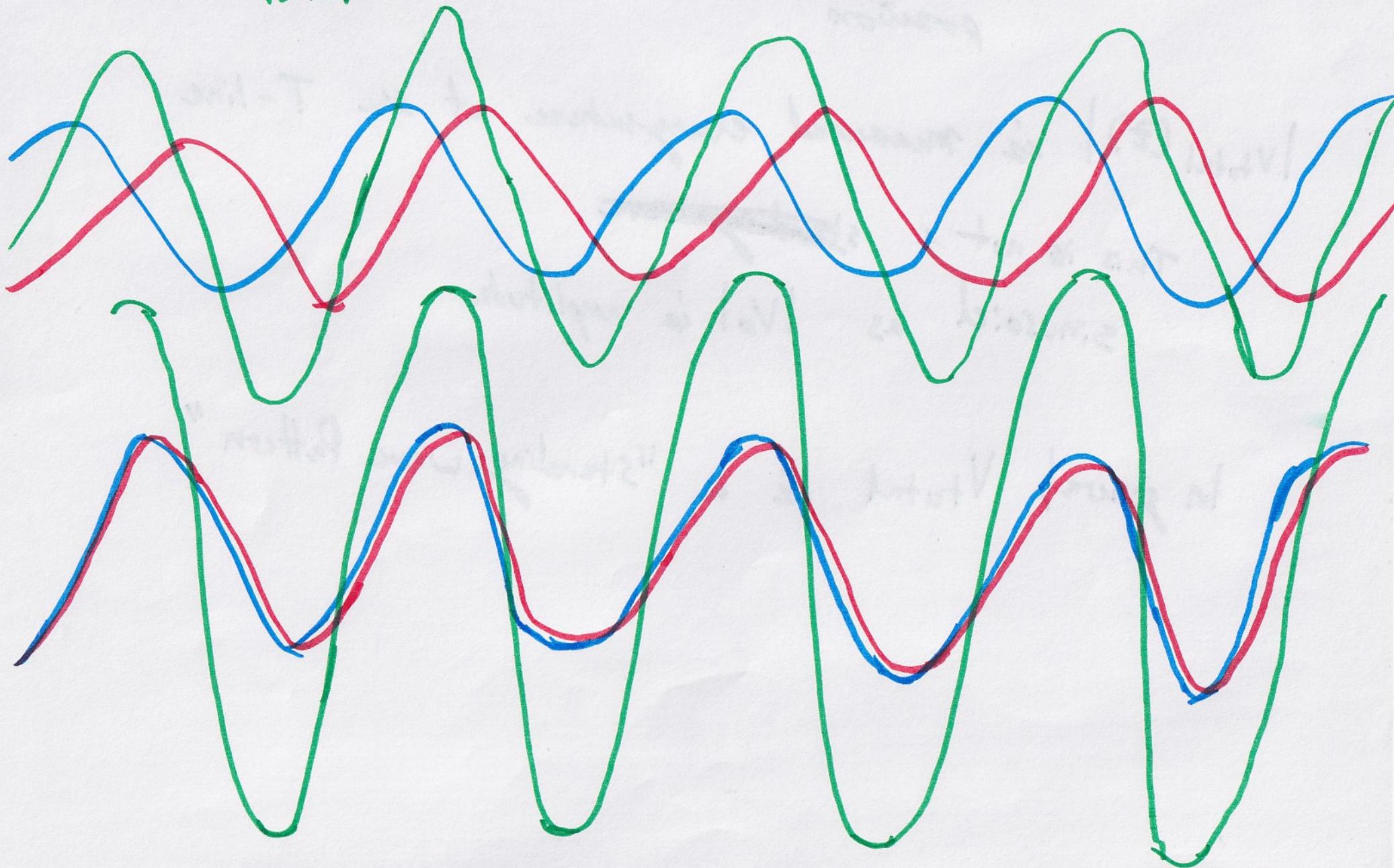

25

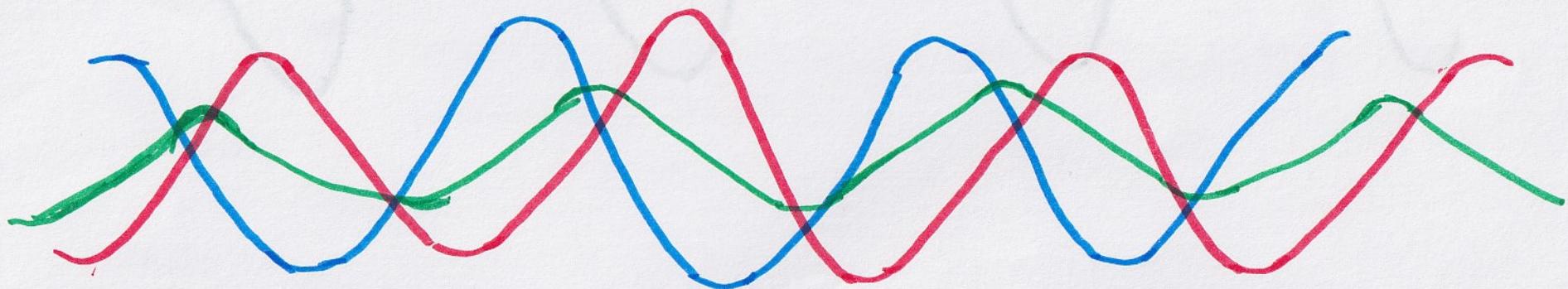

(26)

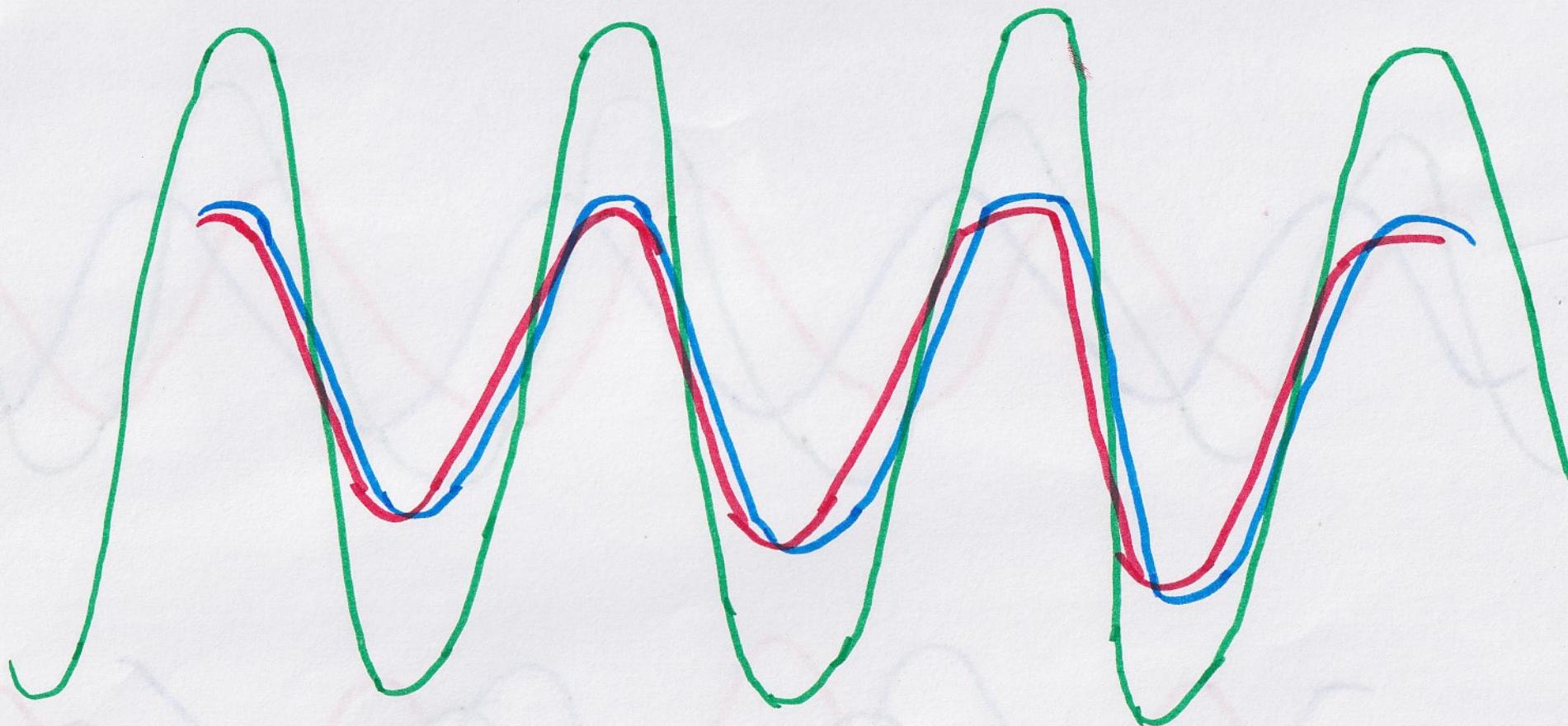

Ex)

$$Z_0 = 100 \Omega$$

$$Z_L = \infty \quad (\text{open ckt})$$


recall  $\beta = \frac{2\pi}{\lambda}$

$$\Gamma = 1$$

$$|V_{\text{total}}(z)| = |V_0| \left| \left( 1 + e^{+2j\beta z} \right) \right|$$


$$|V_{\text{total}}(z)|$$

forward  
wave  
amp

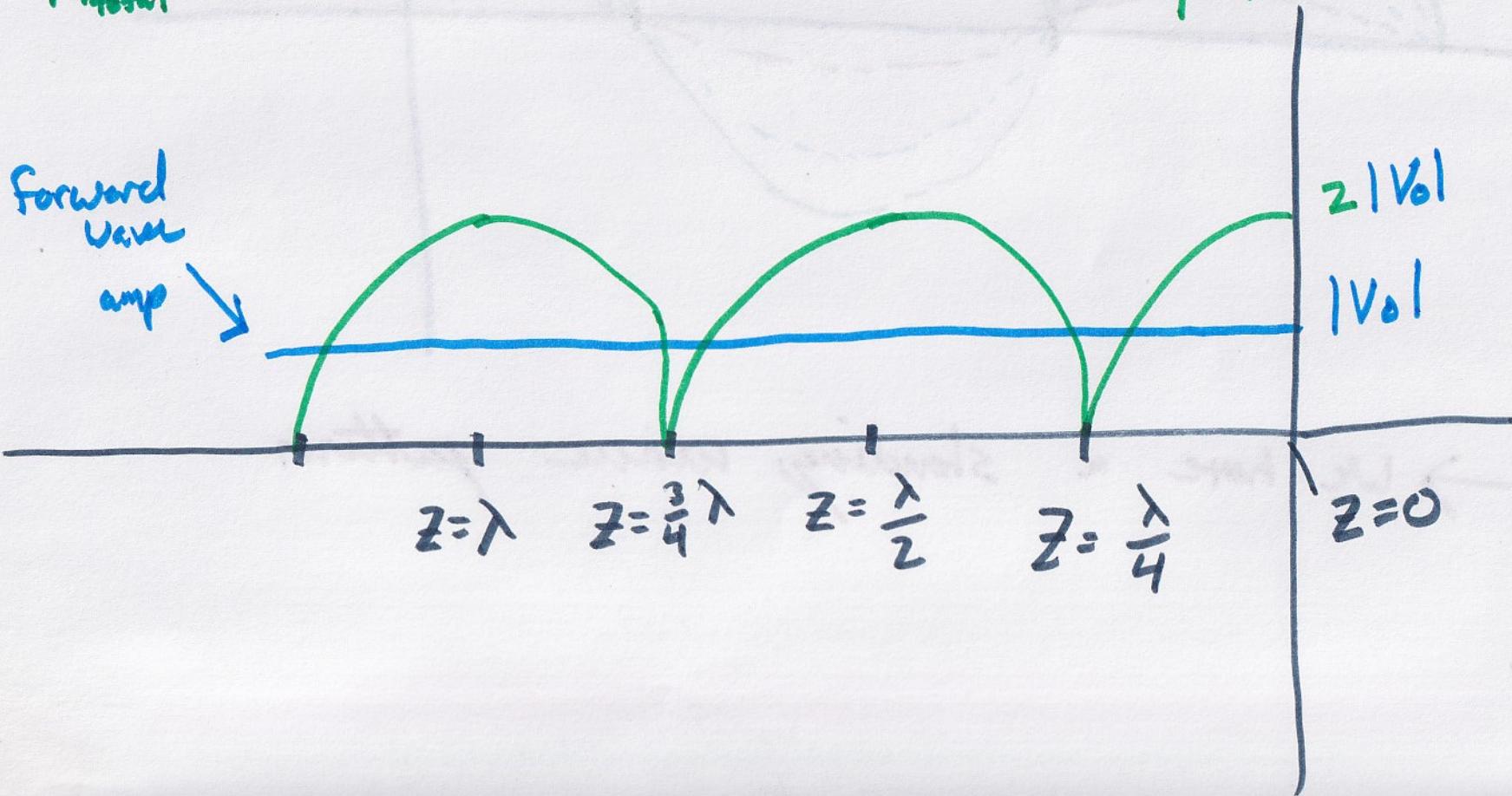

28 We put  $z$  in terms of  $\gamma$ , makes things easier

Amplitude is a function of Position

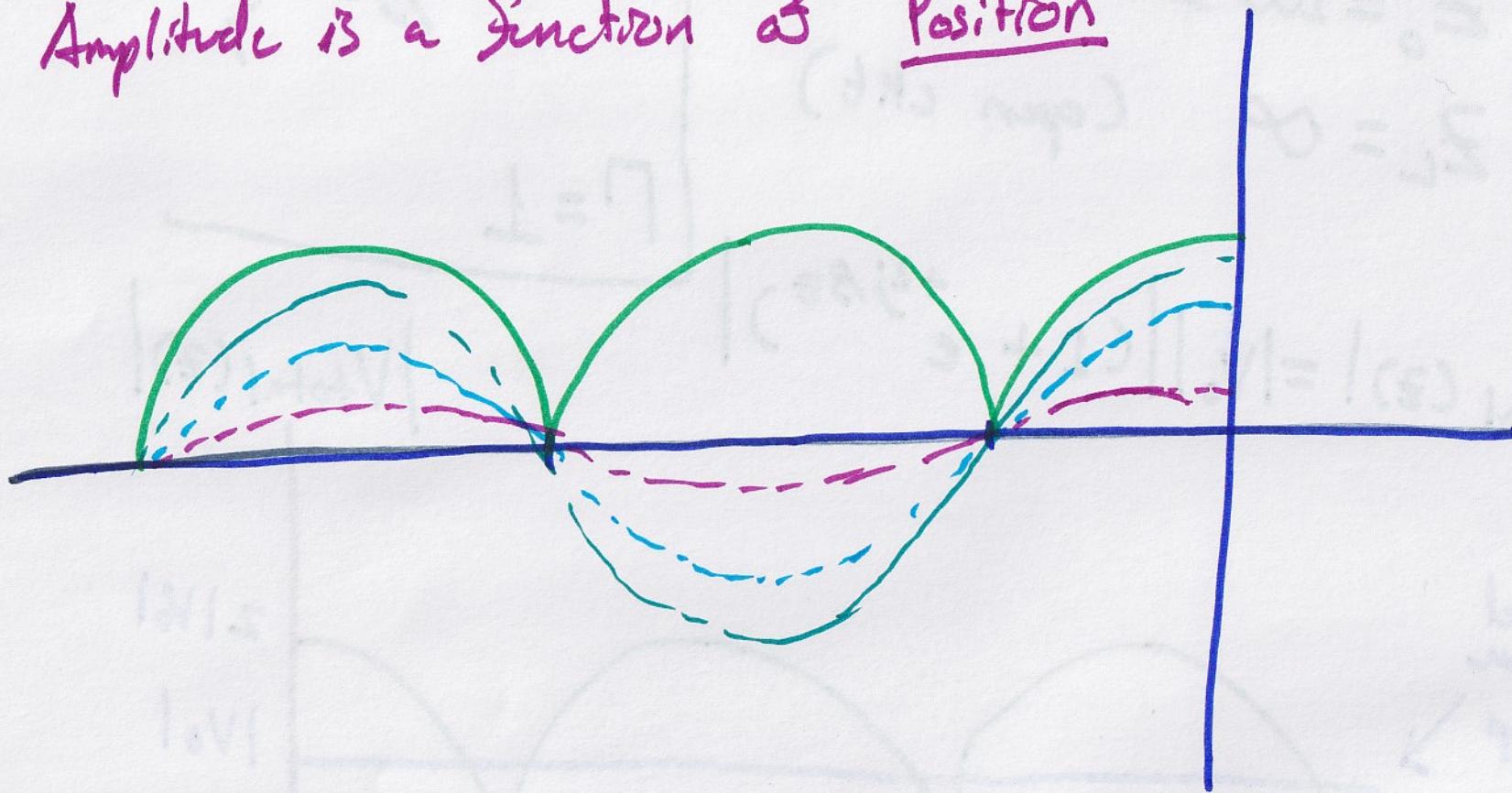

→ We have a standing wave pattern

Ex)

$$|I_{\text{total}}(z)| = \left| \frac{V_0}{Z_0} \right| |(1 - \Gamma e^{+2j\beta z})|$$


→ current standing wave pattern

$$Z_0 = 100$$

$$\Gamma = 1$$

$$Z_L = \infty$$

$$|I_{\text{total}}(z)| = \left| \frac{V_0}{Z_0} \right| |(1 - (1)e^{-Lj\beta z})|$$

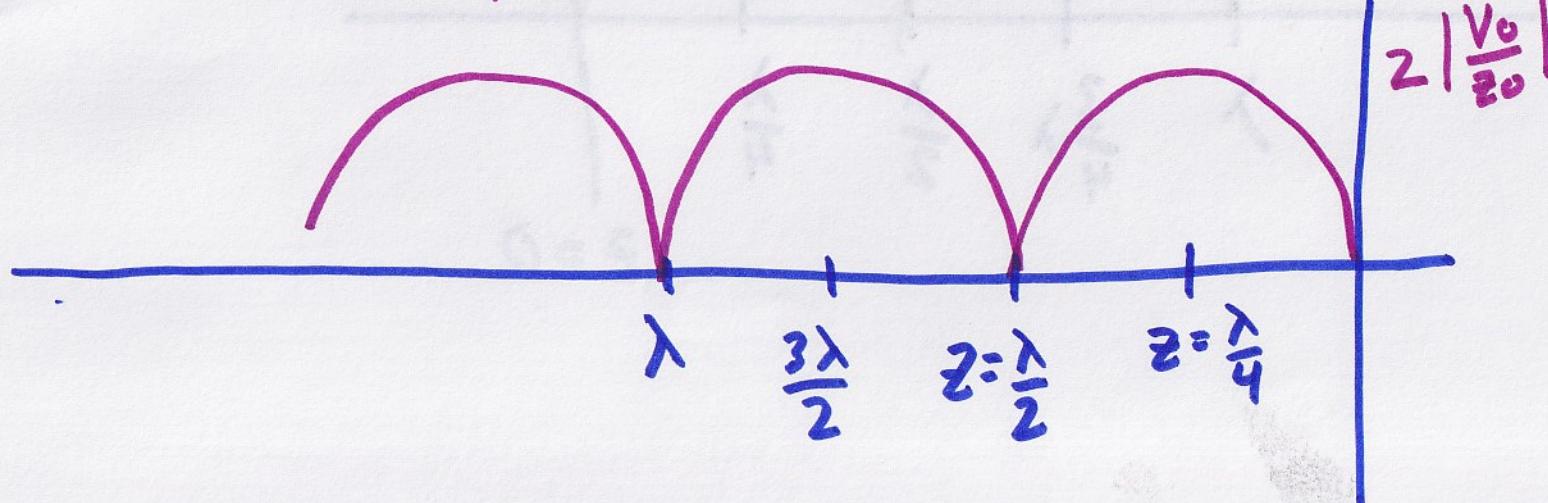

30

Look at short ckt


Ex)

$$Z_0 = 100 \Omega$$

$$Z_L = 0 \quad (\text{short ckt})$$

$$\Gamma = -1$$

$$|V_{\text{total}}(z)| = |V_0| \left| \left( 1 - \Gamma e^{+2j\beta z} \right) \right|$$

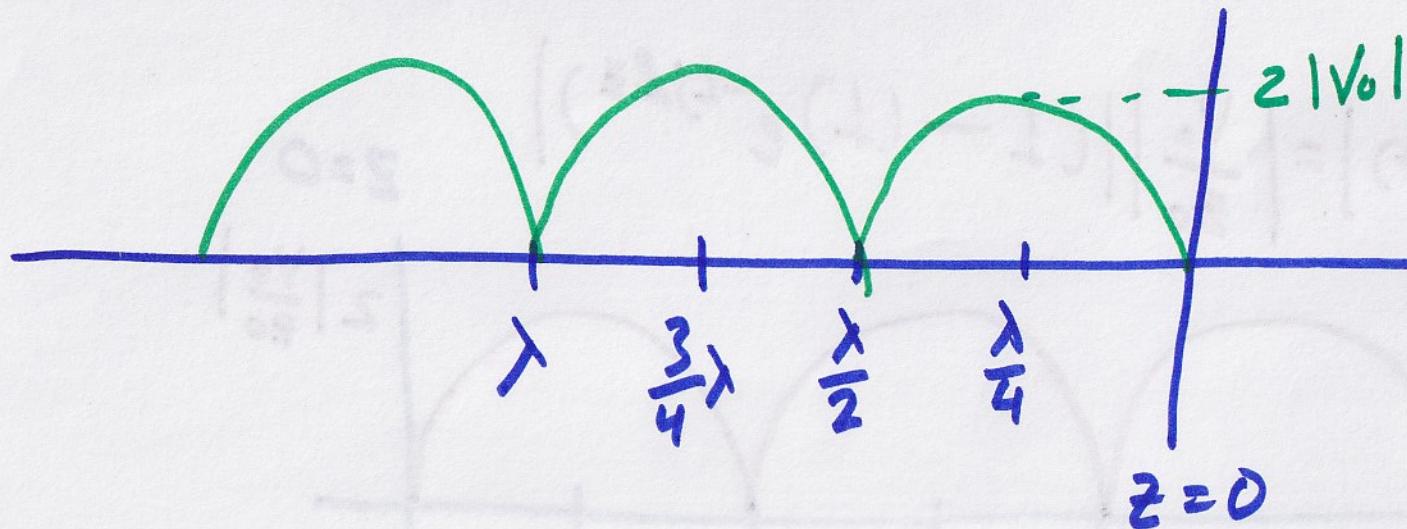

(31)

Standing wave pattern is shifted by  $\frac{\lambda}{2}$

for short ckt

$|I_{\text{total}}(z)|$

