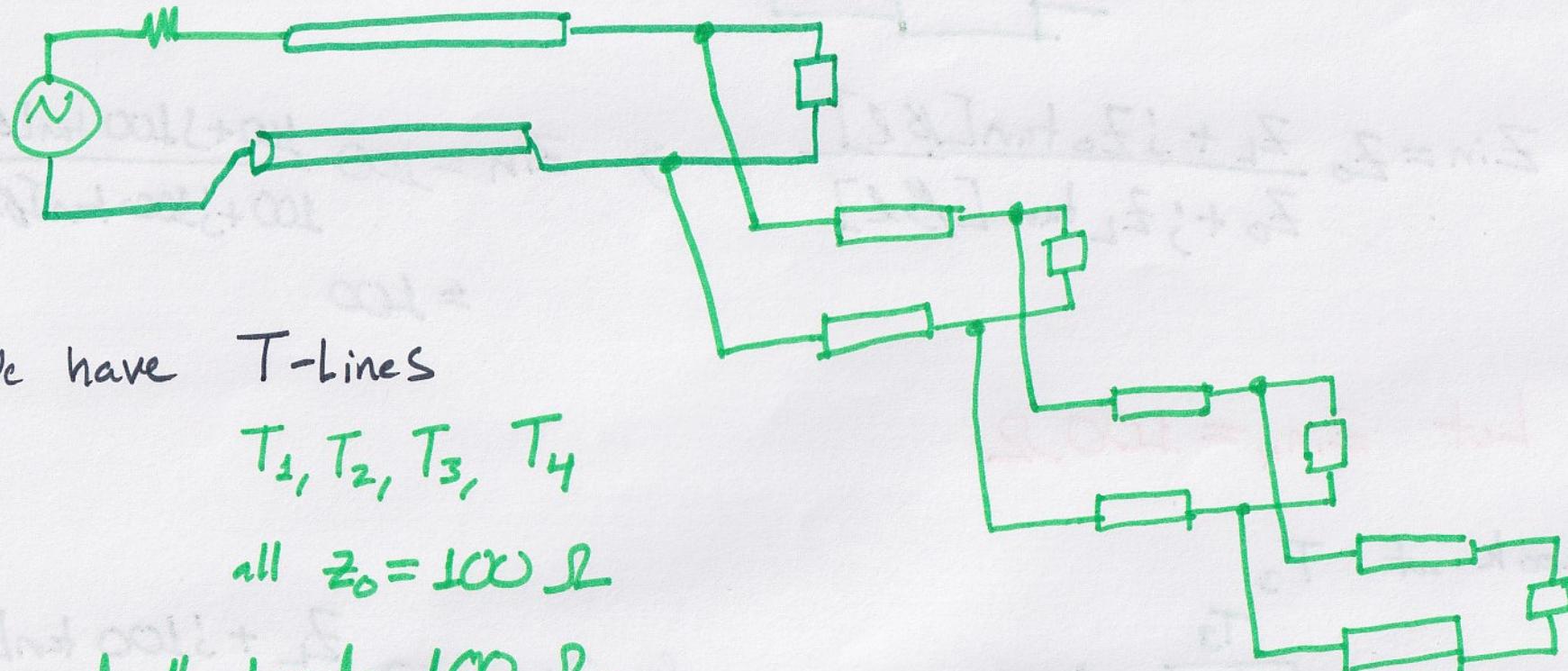


# Fields and Waves I

L5


1

## The Lattice Diagram




So what are the input impedances?

(2)

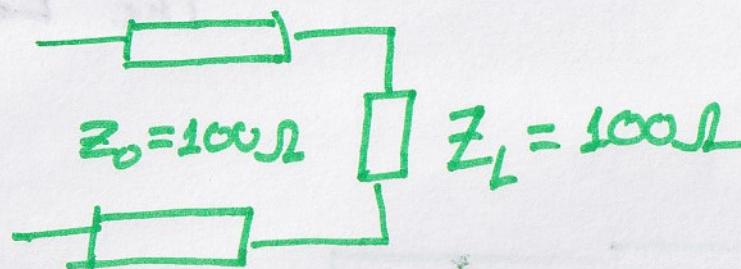Look at  $T_4$ 

$$Z_{in} = Z_o \frac{Z_L + jZ_o \tan[\beta L]}{Z_o + jZ_L \tan[\beta L]} \rightarrow Z_{in} = 100 \frac{100 + j100 \tan[\beta L]}{100 + j100 \tan[\beta L]} = 100$$

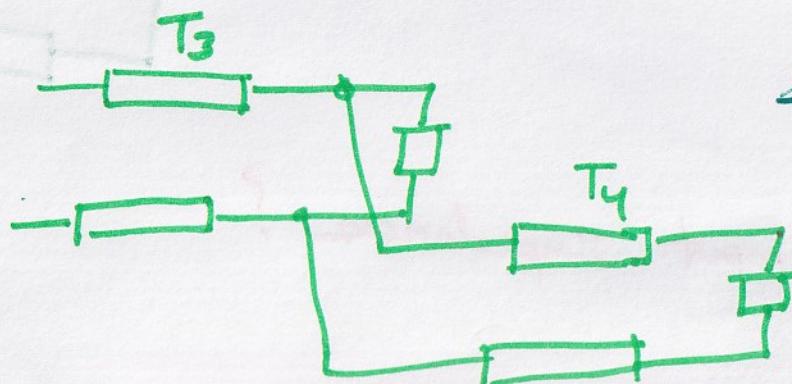Let  $Z_{in_4} = 100\Omega$ Look at  $T_3$ 

$$\text{so } Z_{in_3} = 100 \frac{Z_L + j100 \tan[\beta L]}{100 + jZ_L \tan[\beta L]}$$

(3)

$$Z_L = 100 \parallel 100 = 50 \Omega = Z_{in_4} \parallel 100$$

~~$Z_{in_4} \parallel 100$~~

The Load for  $T_3$  is  $Z_{in_4}$  in parallel with a  $100\Omega$  load.

So what's  $Z_{in_3}$ ?

If we let  $\beta l = 0, 2\pi, 4\pi, \dots$  etc

$$Z_{in_3} = 100 \frac{50\Omega + j100(0)}{100 + j50\Omega(0)} = 50\Omega$$

So Looking at  $T_2$ , the effective Load for  $T_2$  is

$$Z_L = Z_{in_3} \parallel 100\Omega = 50 \parallel 100 \approx 33\Omega$$

So then

$$Z_{in_2} = 100 \frac{33 + j100 \tan(\beta l)}{100 + j33 \tan(\beta l)} = 33\Omega$$

④ So for  $T_1$ , the effective load is

$$Z_{in_2} \parallel 100\Omega = 33 \parallel 100 \simeq 25\Omega$$

If we keep adding loads, eventually the effective loads become

$$\text{effective Loads} = 0$$

$$\text{so then } R = 1$$

Basically, there's a limit to how many people can be on the line.

Let's talk about ~~short~~ short pulses

(5)


We have done AC steady state problems

- Standing waves, SWR
- Input Impedance,  $Z_{in}$


These are not used for pulse Problems

Short pulses


$V_s$

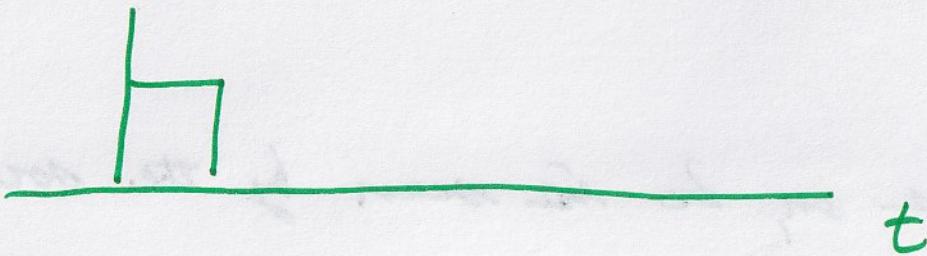

(6)

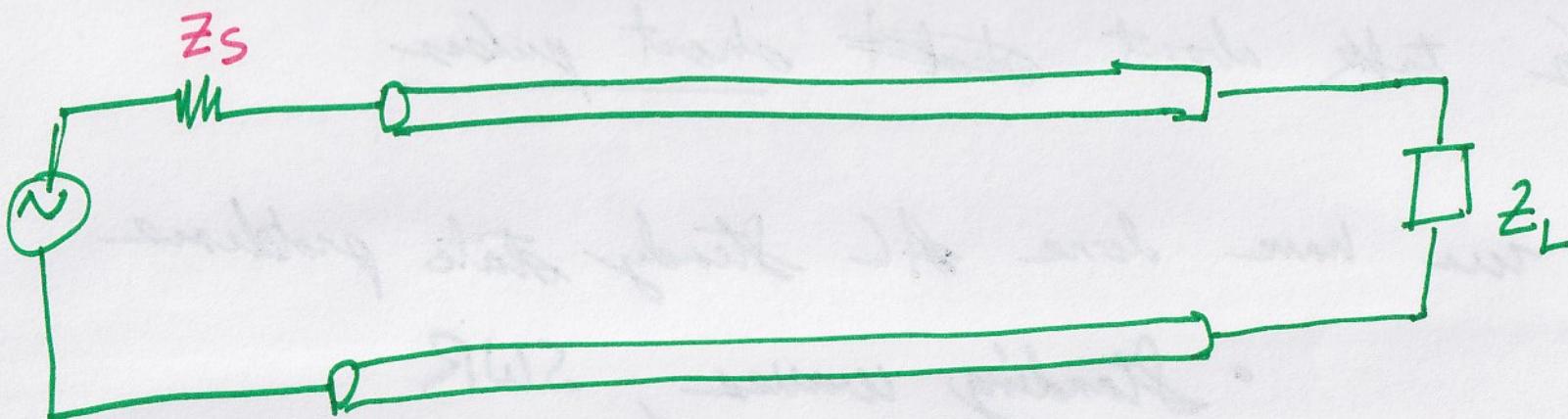

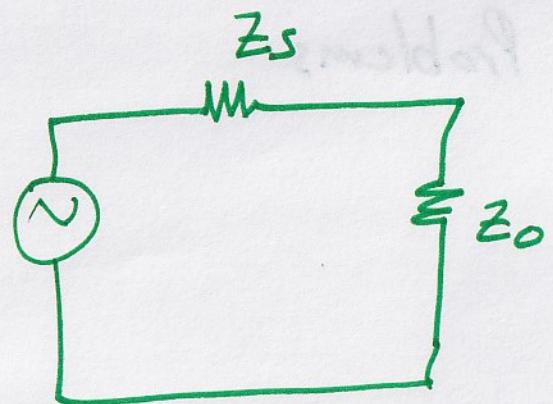At  $t=0$ , what circuit does the source see?



$Z_s$  is the internal Impedance  
 $Z_0$  is the characteristic Impedance

→ When the source turns on,  $Z_0$  is seen by the source circuit

A pulse propagates down the line

(7)

$V_L^+$  ← forward propagating pulse

Ex)

$V_s = 20 \text{ V}$  short Pulse (from the generator)

$$Z_L = Z_0 = Z_s = 50 \Omega$$



So Then

$$V_L^+ = \frac{Z_0}{Z_0 + Z_s} V_s = 10 \text{ V}$$

What happens when the pulse reaches the load?

(8)

$$V_{in} \quad (V_M = \frac{Z_0}{Z_0 + Z_M} V_S)$$

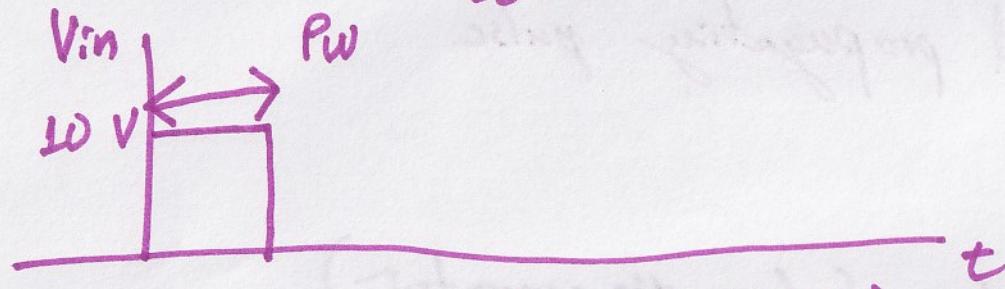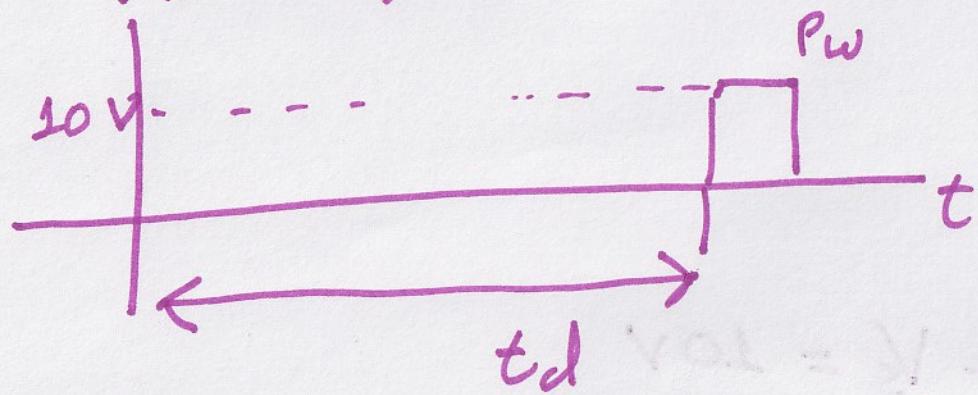(  $V_{in}$  has the amplitude of  $V_L^+$  ) $V_L$  (Voltage at the Load,  $V_L$ )

We see that the pulse takes  $t_d$  time to reach the Load. So it's important to note,

a short pulse implies  $\rightarrow$  pulselwidth  $\ll t_d$

(9)


Ex)

$$Z_s = 150 \Omega$$


$$Z_o = Z_L = 50 \Omega$$

$$V_I^+ = \frac{50}{50 + 150} (20 V) = 5 V$$

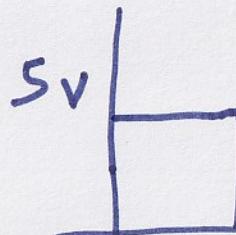$V_{\text{source}} (V_{\text{in}})$  ( $V_I^+$ )



$V_{\text{load}}$

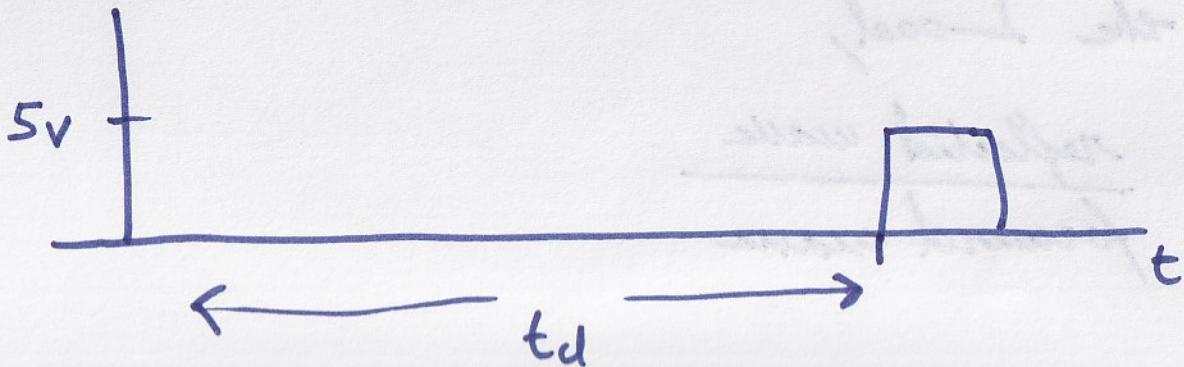

(10)

Ex)

$$Z_L = 133 \Omega$$

$$Z_0 = Z_s = 50 \Omega$$

$$V_s = 20V$$

at  $t=0$ 

$$V_L^+ = \frac{50}{50+50} (20) = 10V$$

$$\Gamma_L = \frac{133 - 50}{133 + 50} = \frac{83}{183} \approx 0.45$$

(reflection coefficient for the Load)

When the pulse hits the Load,

$$\Gamma_L = \frac{|V_-|}{|V_+|} \quad \frac{\text{reflected wave}}{\text{forward wave}}$$

$V_1^+$  → first forward pulse

$V_1^-$  → first reflected pulse

$$V_L = V_1^+ + V_1^- = V_1^+ (1 + \Gamma)$$




We know  $V_1^- \approx 4.5V$   
(from the  $\Gamma_L$ )

So then we can say  $V_{L1} = 14.5V$

The First observation at the Load

We have constructive interference at the Load  
for  $+ \Gamma$


12

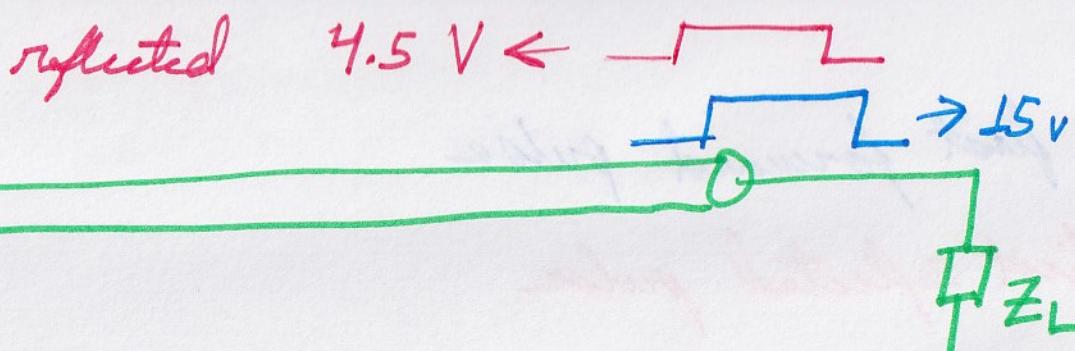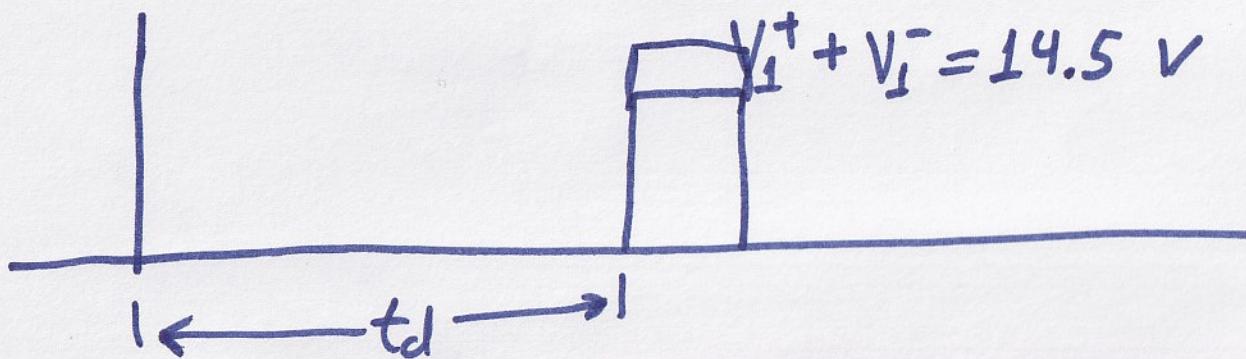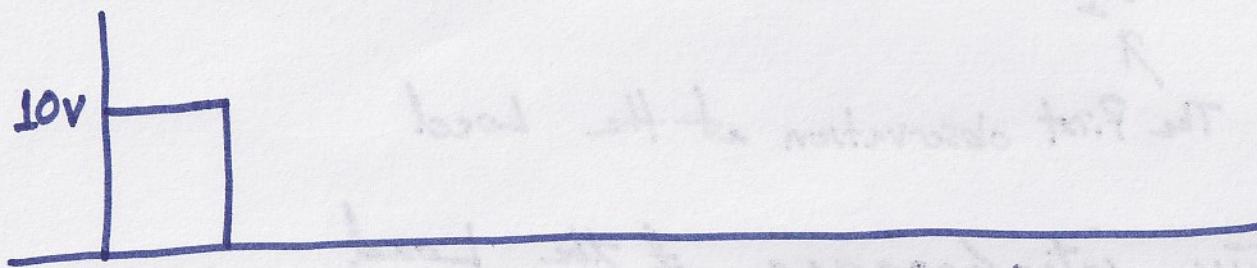 $V_s$  ( $V_{in}$ )

4.5V reflected is added to the Voltage at the Load. At  $2t_d$ , ~~14.5V~~ with 4.5V goes back to the source

so far  $t >> t_d$

13

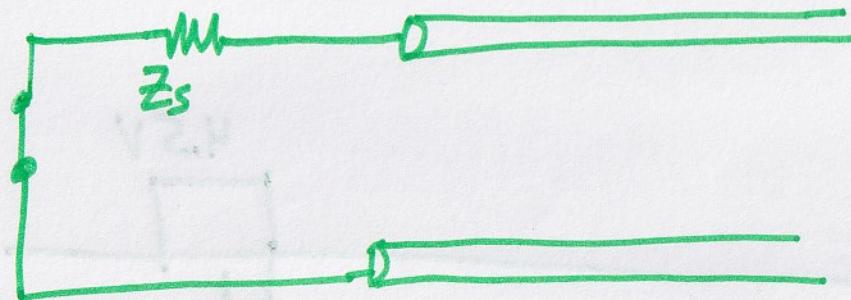

well now,  $\Gamma_s$  this is the reflection coefficient at the source end of the Line


$$\Gamma_s = \frac{Z_s - Z_0}{Z_s + Z_0}$$

$Z_0 = Z_s$  we have a 'Load match' for the problem

$$\text{so } \Gamma_s = 0$$


L4

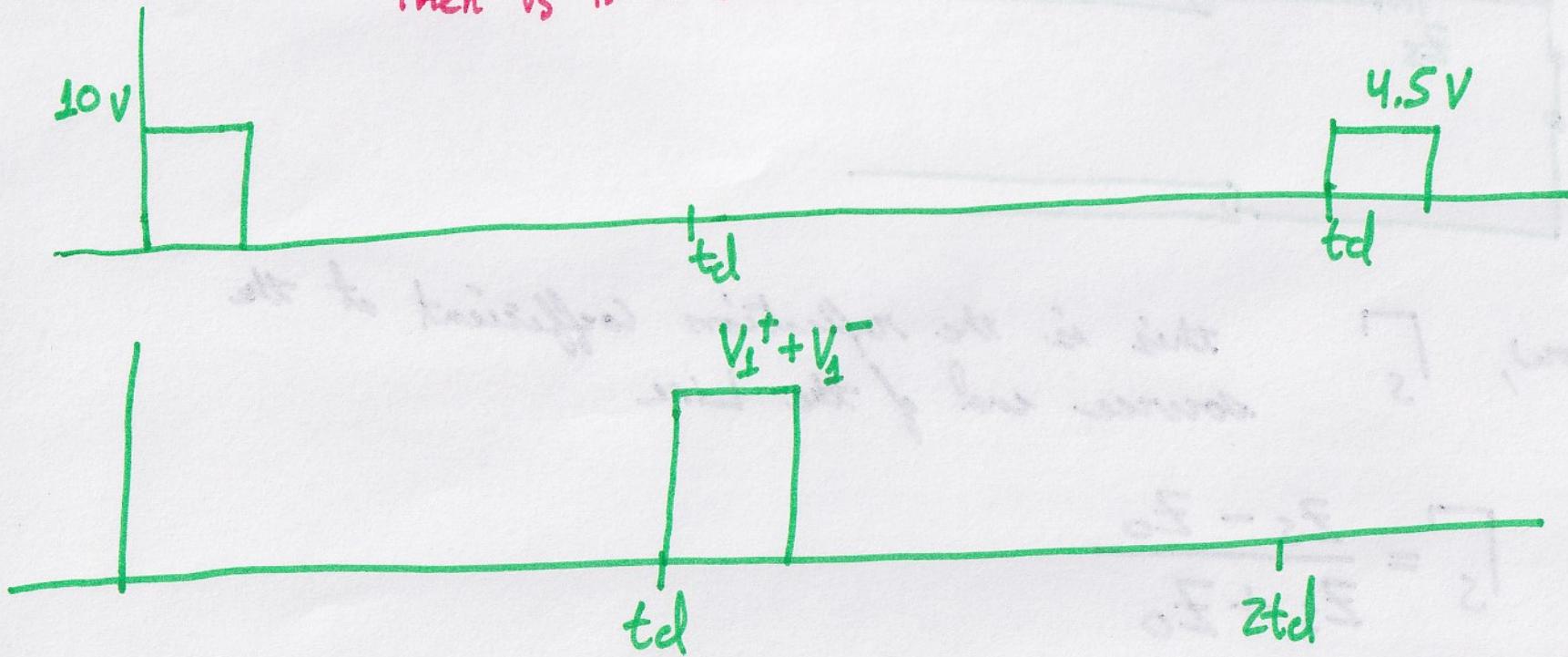$V_s$  ( $V_{in}$ )  $V_m$  ( $V_s$ ) is the Voltage going into the T-Line  
Then  $V_s$  is as follows





The reflected pulse comes back to hit the source at  $2t_d$   
(4.5V reflected reflected to the source)

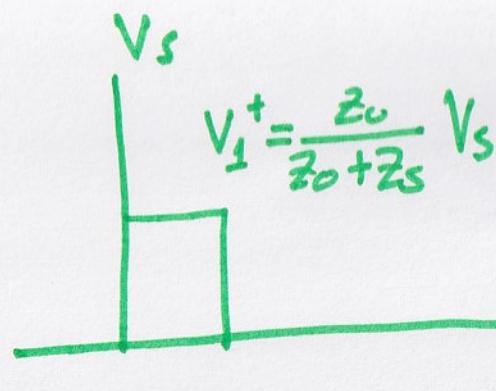as  $S = 0$  there is no reflected Voltage to the Load


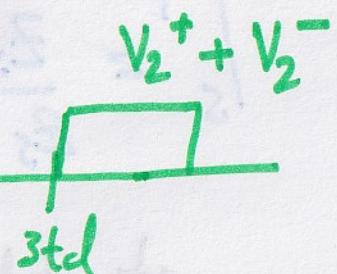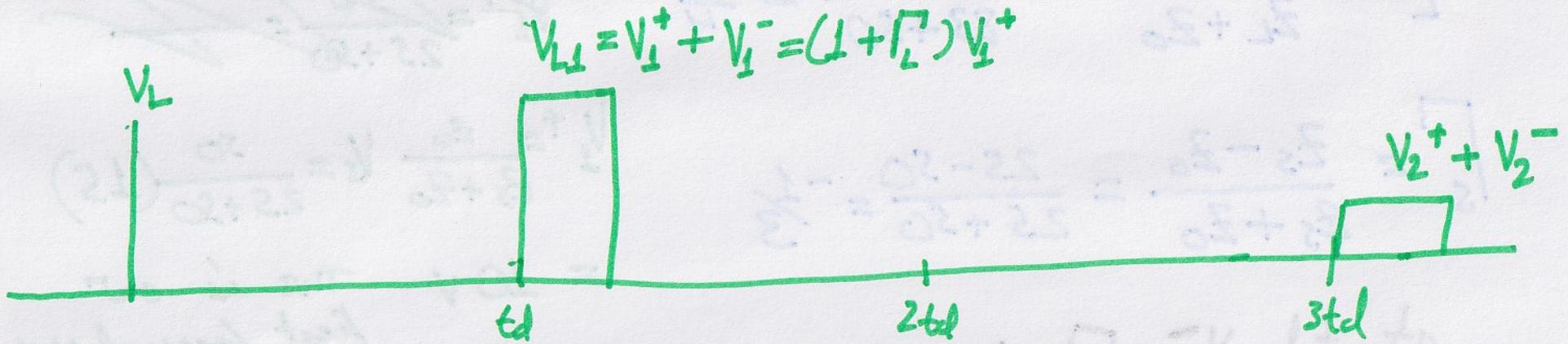
$$\begin{aligned} V_L^- + V_L^+ &= \Gamma_L V_L^+ + \Gamma_S V_L^- \\ &= \Gamma_L V_L^+ + \frac{1}{\Gamma} (\Gamma_L V_L^+) \\ &= (\Gamma_L + \Gamma_S \Gamma_L) V_L^+ \end{aligned}$$



(16)

## Another Example

$$Z_0 = 50 \Omega, Z_L = 83 \Omega, Z_S = 25$$

$$V_S = 15V$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{83 - 50}{83 + 50} = \frac{1}{4}$$

~~$$V_I^+ = \frac{50}{25 + 50} = \frac{1}{3}$$~~


$$\Gamma_S = \frac{Z_S - Z_0}{Z_S + Z_0} = \frac{25 - 50}{25 + 50} = -\frac{1}{3}$$

$$V_I^+ = \frac{Z_0}{Z_S + Z_0} V_S = \frac{50}{25 + 50} (15)$$

$= 10V$  This is our  
first forward wave  
This is the first  
reflected wave


$$\text{at } 2td \quad V_I^+ = \Gamma_S V_I^- = \left(-\frac{1}{3}\right)(2.5) \approx -0.83 \quad \text{This is the 2nd forward wave}$$
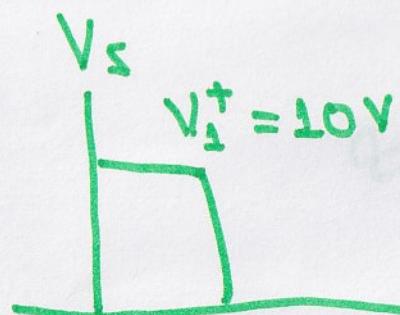
$$\text{at } 3td \quad V_I^- = \Gamma_L V_I^+ = \left(\frac{1}{4}\right)(-0.83) \approx -0.21 \quad \text{This is the 2nd reflected wave}$$




$$V_1^+ = 10 \text{ V}$$
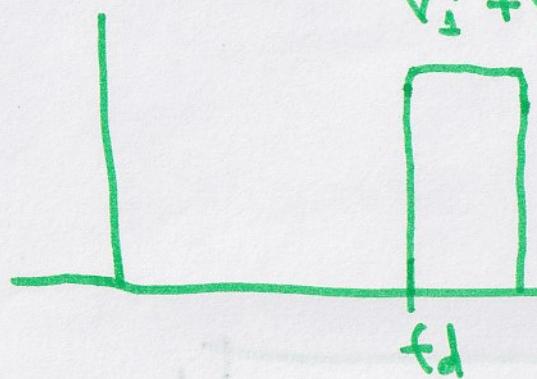
$$V_1^- + V_2^+ = 2.5 - 0.83 = 1.66 \text{ V}$$




$$V_1^+ + V_1^- = 10 + 2.5 \\ = 12.5 \text{ V}$$

$$V_2^+ + V_2^- = -1.04$$

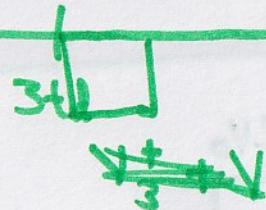

18

# Goofy Case Study

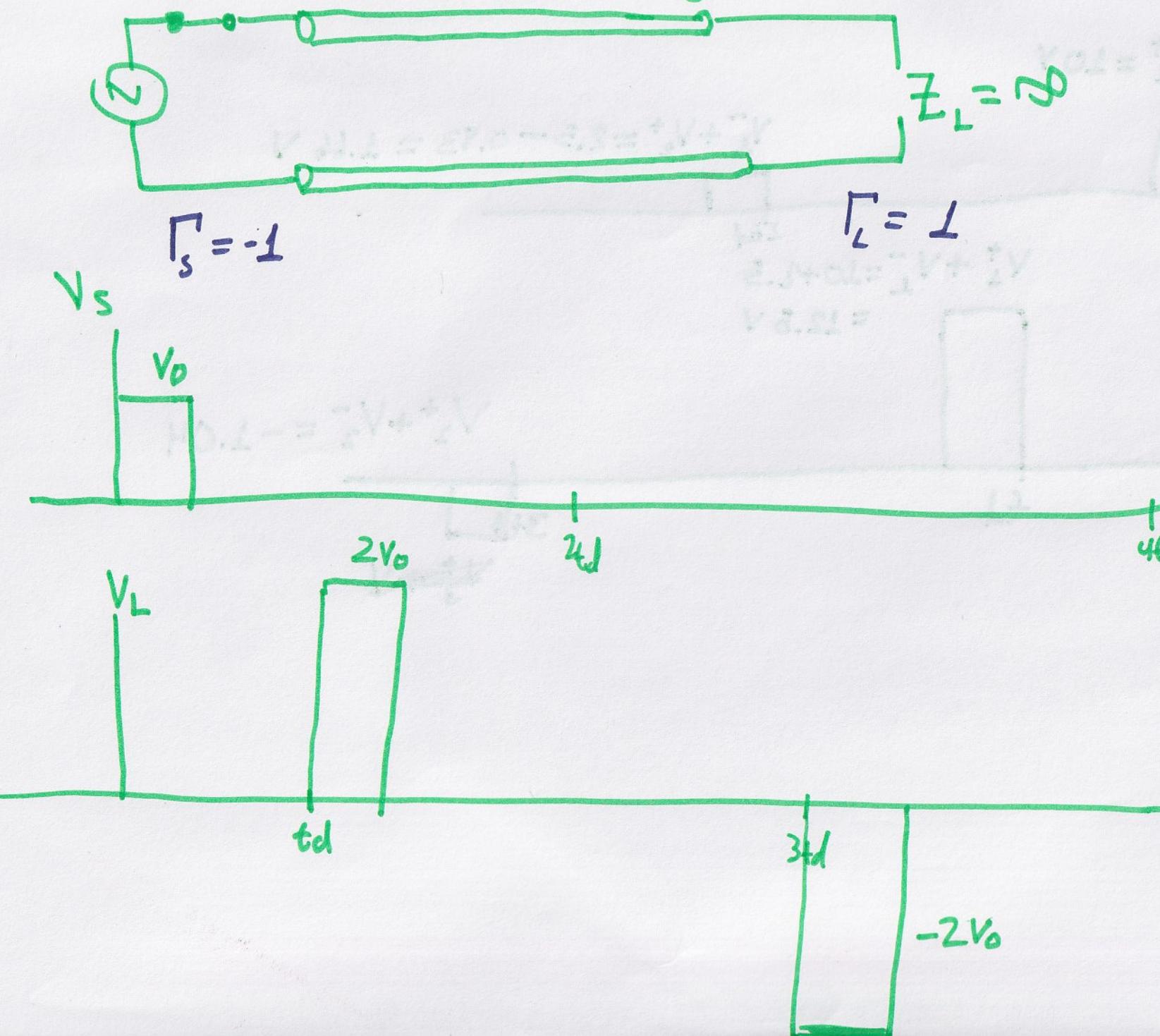


# Bounce Diagram (Lattice Diagram)

$$Z_0 = 50, Z_L = 83, Z_S = 25 \quad V_S = 15 \text{ V pulse}$$

$$\Gamma_L = \frac{1}{4} \quad \Gamma_S = -\frac{1}{3}$$

We have another way to look at this

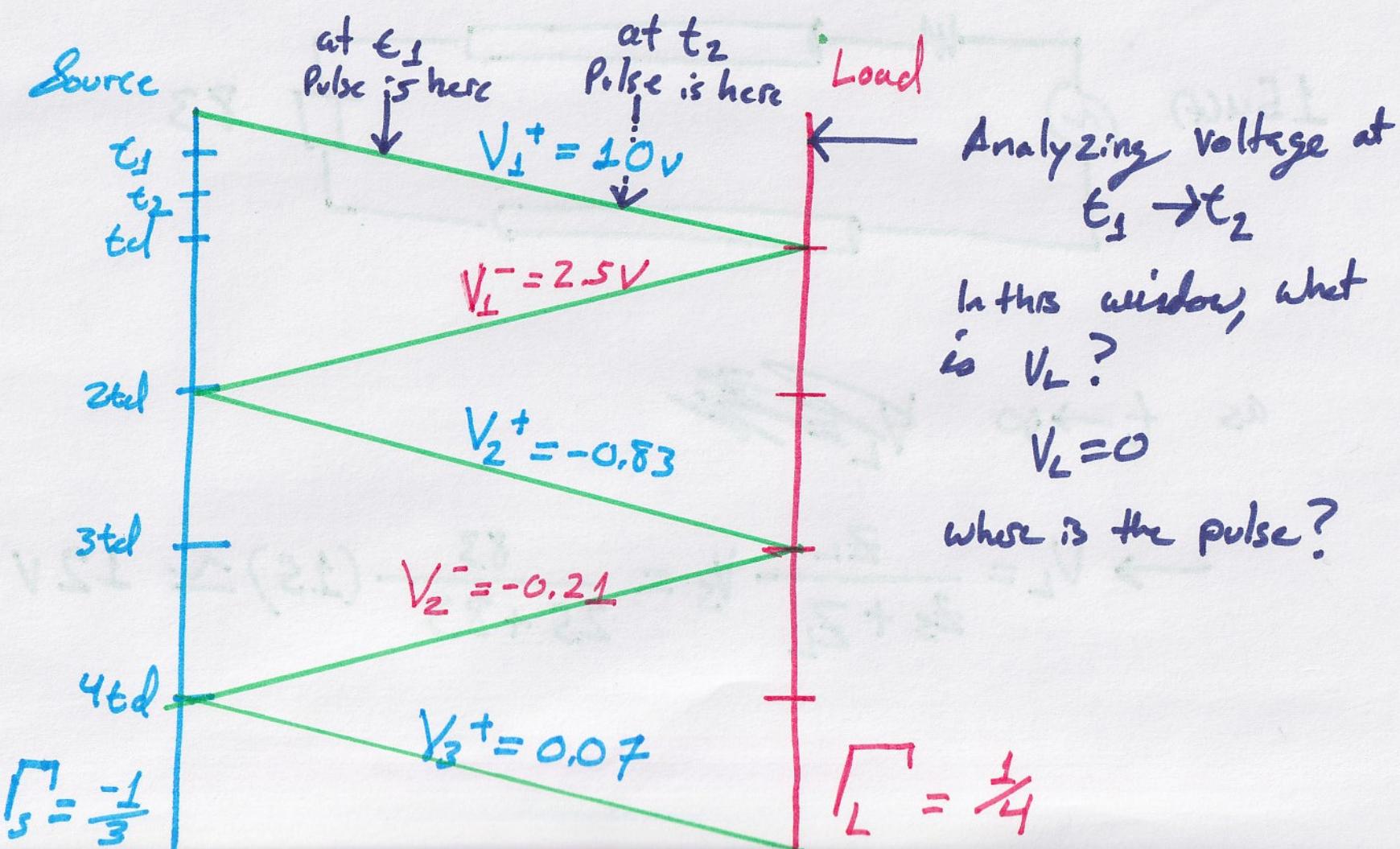


20

Long PulseExample is Step Function

→ turn a switch on and leave it on.

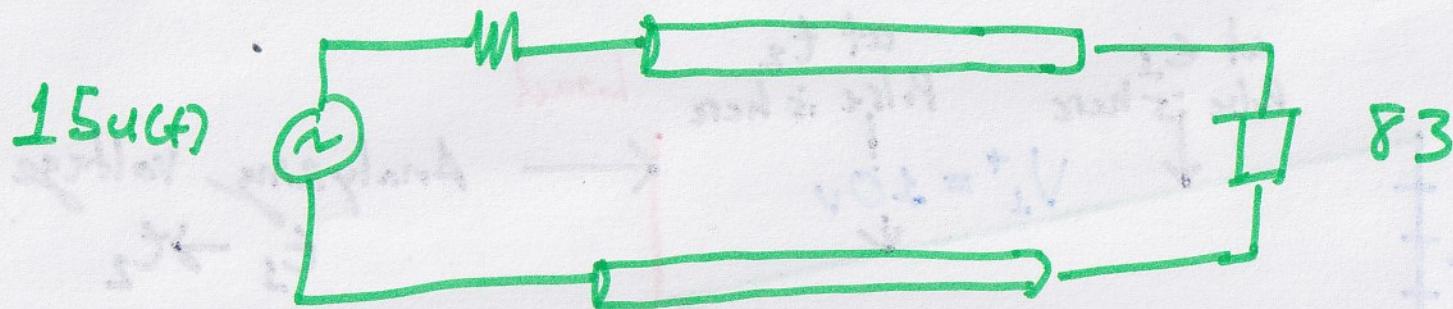$V_s = 15 \text{ V}$ , turned on at  $t=0$  (stays on)




as  $t \rightarrow \infty$   ~~$V_L = ?$~~


$$\rightarrow V_L = \frac{Z_L}{Z_S + Z_L} V_s = \frac{83}{25 + 83} (15) \approx 12 \text{ V}$$

Here's how this happens

21

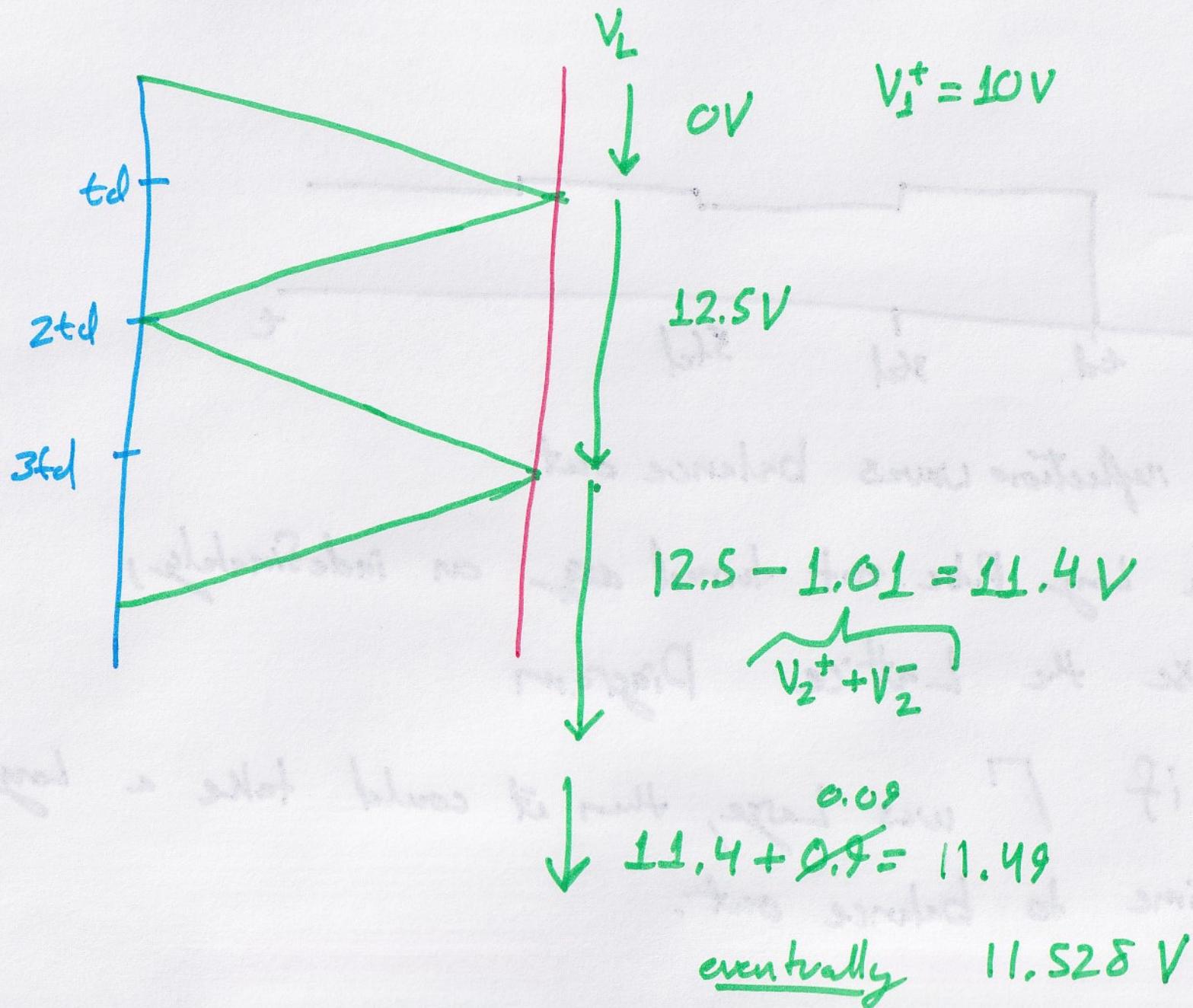

(22) Eventually we converge to DC value

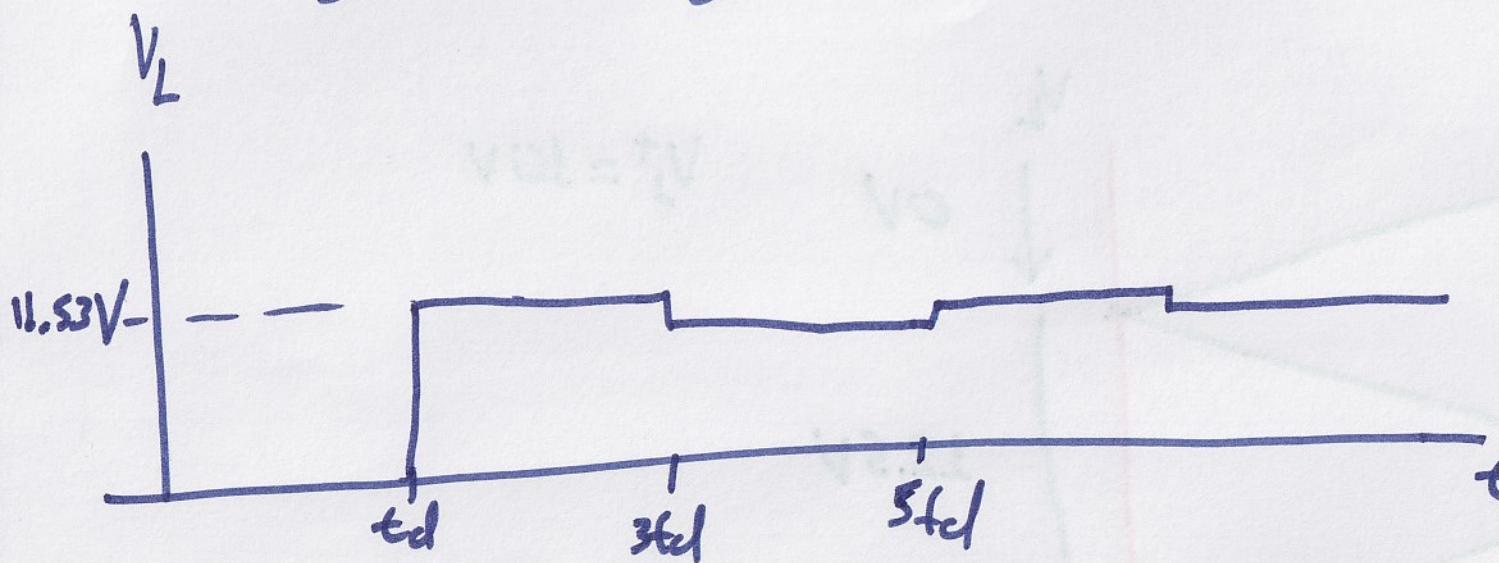

The reflection waves balance out

For a Long Pulse not turned off on indefinitely,  
use the Lattice Diagram

if  $\Gamma$  was Large, then it could take a long  
time to balance out.