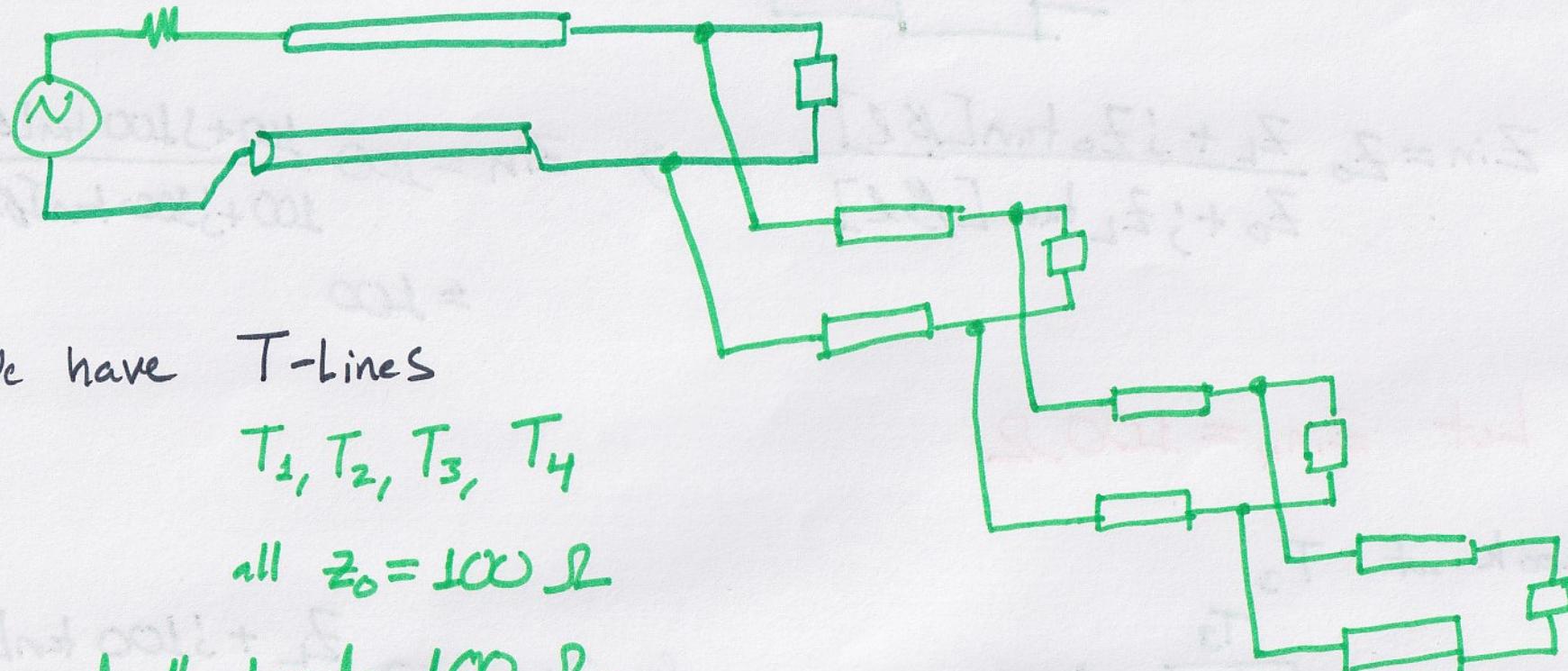


Fields and Waves I

L5

1

The Lattice Diagram



We have T-Lines


$$T_1, T_2, T_3, T_4$$

$$\text{all } Z_0 = 100 \Omega$$


$$\text{and all Loads } 100 \Omega$$

So what are the input impedances?

(2)

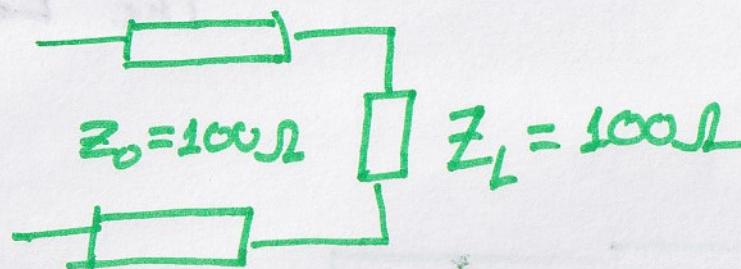Look at T_4 

$$Z_{in} = Z_o \frac{Z_L + jZ_o \tan[\beta L]}{Z_o + jZ_L \tan[\beta L]} \rightarrow Z_{in} = 100 \frac{100 + j100 \tan[\beta L]}{100 + j100 \tan[\beta L]} = 100$$

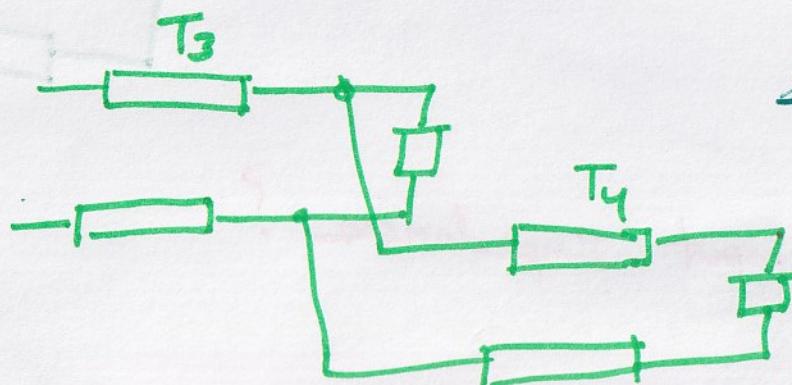Let $Z_{in_4} = 100\Omega$ Look at T_3 

$$\text{so } Z_{in_3} = 100 \frac{Z_L + j100 \tan[\beta L]}{100 + jZ_L \tan[\beta L]}$$

(3)

$$Z_L = 100 \parallel 100 = 50 \Omega = Z_{in_4} \parallel 100$$

~~$Z_{in_4} \parallel 100$~~

The Load for T_3 is Z_{in_4} in parallel with a 100Ω load.

So what's Z_{in_3} ?

If we let $\beta l = 0, 2\pi, 4\pi, \dots$ etc

$$Z_{in_3} = 100 \frac{50\Omega + j100(0)}{100 + j50\Omega(0)} = 50\Omega$$

So Looking at T_2 , the effective Load for T_2 is

$$Z_L = Z_{in_3} \parallel 100\Omega = 50 \parallel 100 \approx 33\Omega$$

So then

$$Z_{in_2} = 100 \frac{33 + j100 \tan(\beta l)}{100 + j33 \tan(\beta l)} = 33\Omega$$

④ So for T_1 , the effective load is

$$Z_{in_2} \parallel 100\Omega = 33 \parallel 100 \approx 25\Omega$$

If we keep adding loads, eventually the effective loads become

$$\text{effective Loads} = 0$$

$$\text{so then } R = 1$$

Basically, there's a limit to how many people can be on the line.

Let's talk about ~~short~~ short pulses

(5)


We have done AC steady state problems

- Standing waves, SWR
- Input Impedance, Z_{in}


These are not used for pulse Problems

Short pulses


V_s

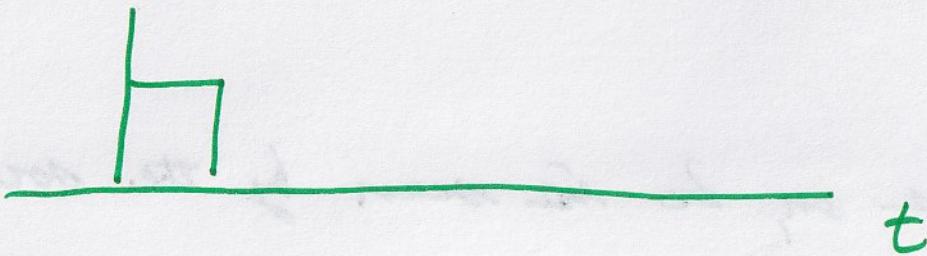

⑥

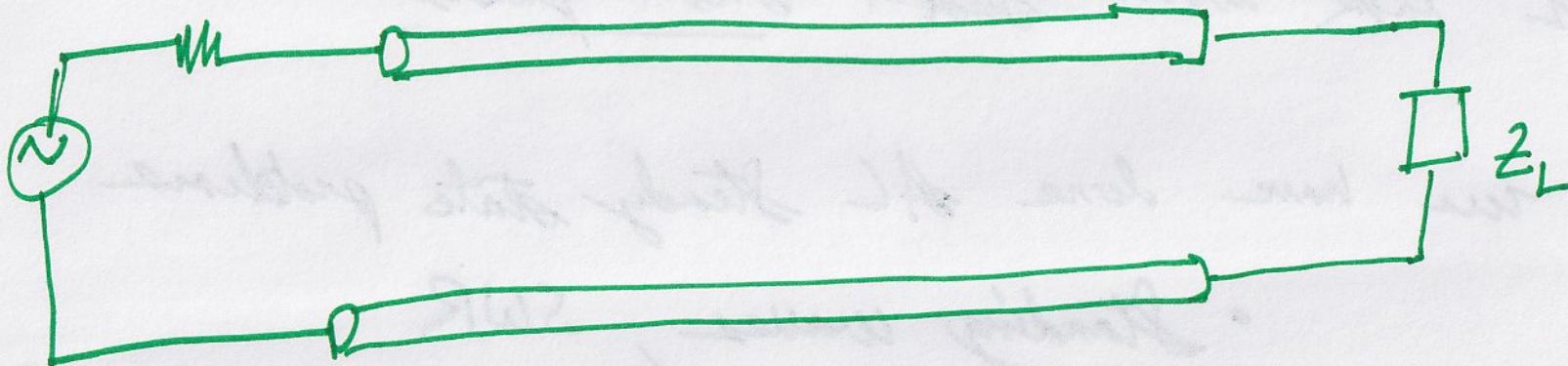

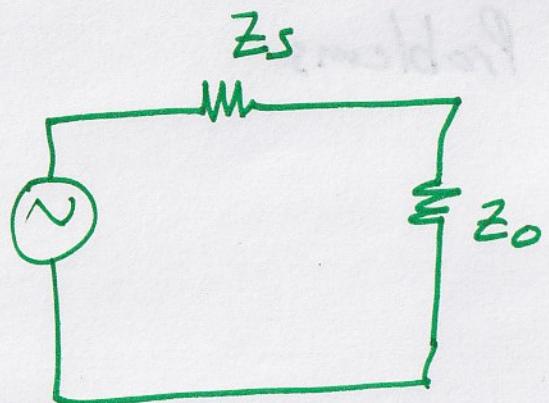At $t=0$, what circuit does the source see?



Z_s is the internal Impedance
 Z_0 is the characteristic Impedance

→ When the source turns on, Z_0 is seen by the source circuit

A pulse propagates down the line

(7)

V_L^+ ← forward propagating pulse

Ex)

$V_s = 20 \text{ V}$ short Pulse (from the generator)

$$Z_L = Z_0 = Z_s = 50 \Omega$$

So Then


$$V_L^+ = \frac{Z_0}{Z_0 + Z_s} V_s = 10 \text{ V}$$

What happens when the pulse reaches the load?


(8)

$$V_{in} \quad (V_M = \frac{Z_0}{Z_0 + Z_M} V_S)$$

(V_{in} has the amplitude of V_L^+)

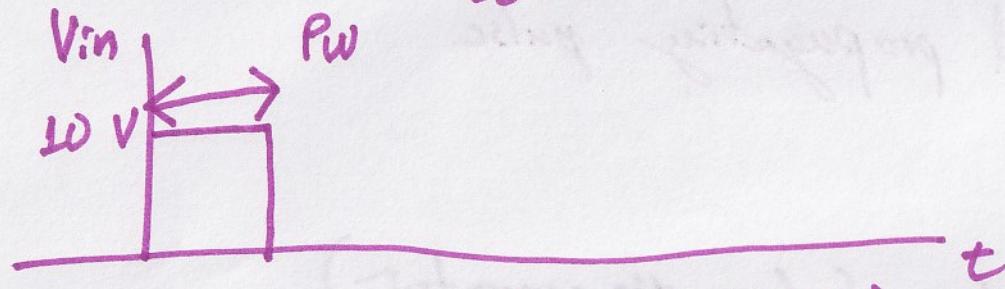

V_L (Voltage at the Load, V_L)

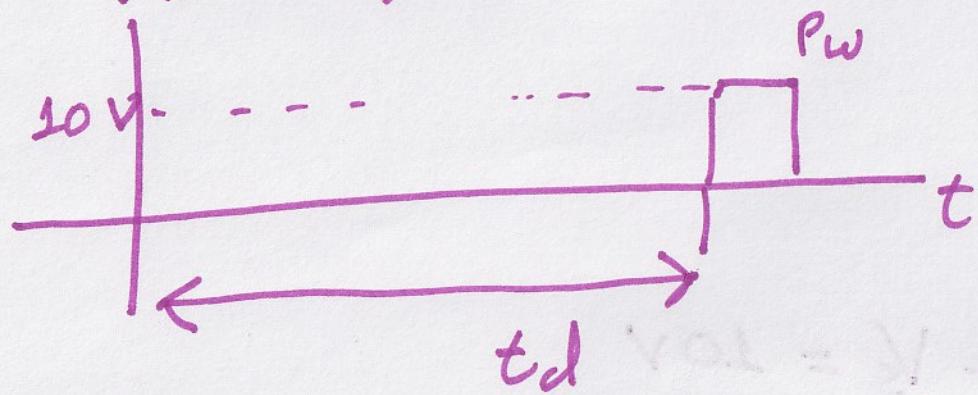

We see that the pulse takes t_d time to reach the Load. So it's important to note,

a short pulse implies \rightarrow pulselwidth $\ll t_d$

(9)

Ex)


$$Z_s = 150 \Omega$$

$$Z_o = Z_L = 50 \Omega$$


$$V_I^+ = \frac{50}{50 + 150} (20 V) = 5 V$$

$$V_{OL} = (20 - \frac{50}{50+50}) = 15 V$$

V_{source} (V_{in})

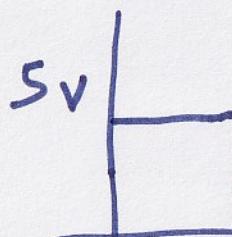

V_{load}

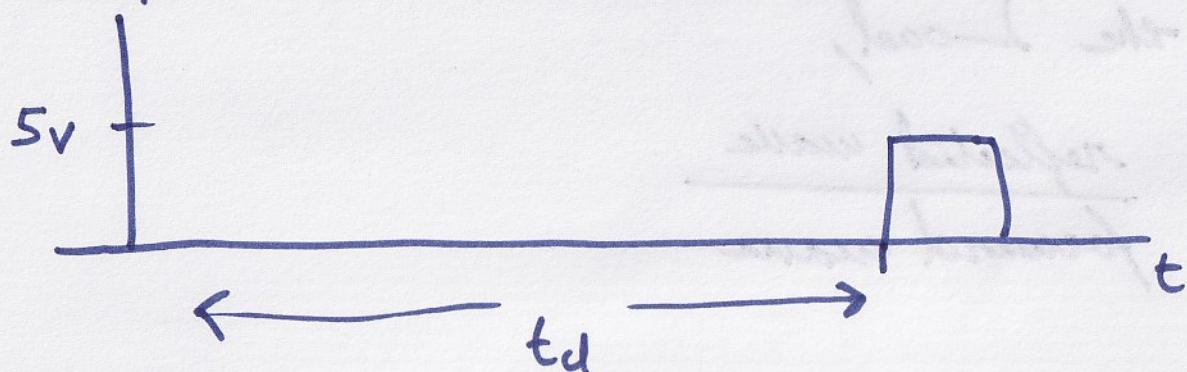

(10)

Ex)

$$Z_L = 133 \Omega$$

$$Z_0 = Z_s = 50 \Omega$$

$$V_s = 20V$$

at $t=0$

$$V_L^+ = \frac{50}{50+50} (20) = 10V$$

$$\Gamma_L = \frac{133 - 50}{133 + 50} = \frac{83}{183} \approx 0.45$$

(reflection coefficient for the Load)

When the pulse hits the Load,

$$\Gamma_L = \frac{|V_-|}{|V_+|} \quad \frac{\text{reflected wave}}{\text{forward wave}}$$

V_1^+ → first forward pulse

V_1^- → first reflected pulse

$$V_L = V_1^+ + V_1^- = V_1^+ (1 + \Gamma)$$




We know $V_1^- \approx 4.5V$
(from the Γ_L)

So then we can say $V_{L1} = 14.5V$

The First observation at the Load

We have constructive interference at the Load
for $+ \Gamma$


12

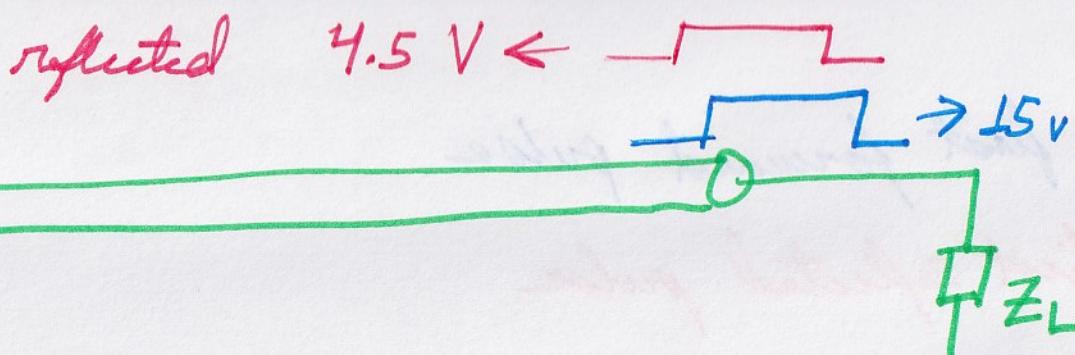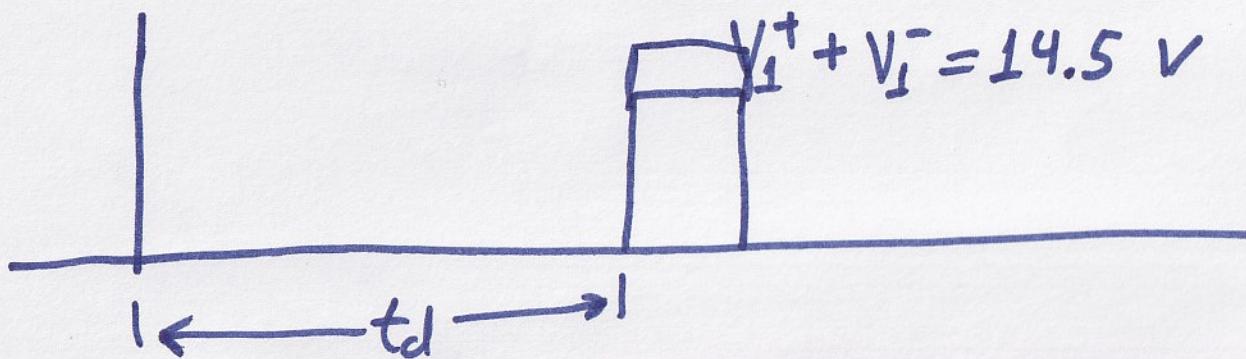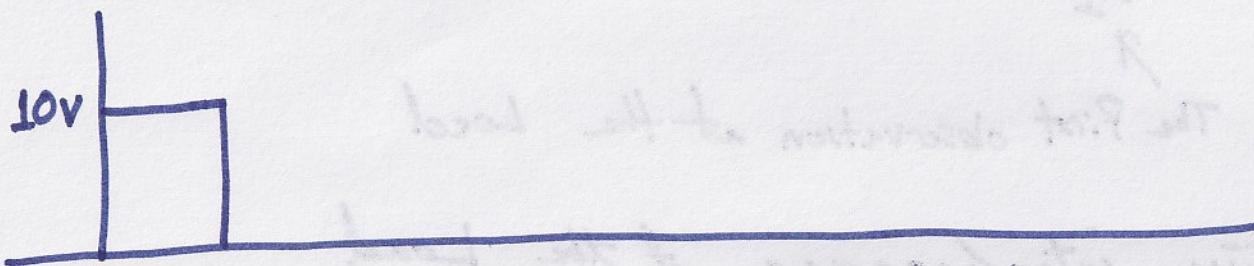 V_s (V_{in})

4.5 V reflected is added to the Voltage at the Load. At $2t_d$, ~~14.5V~~ with 4.5V goes back to the source

so far $t >> t_d$

13

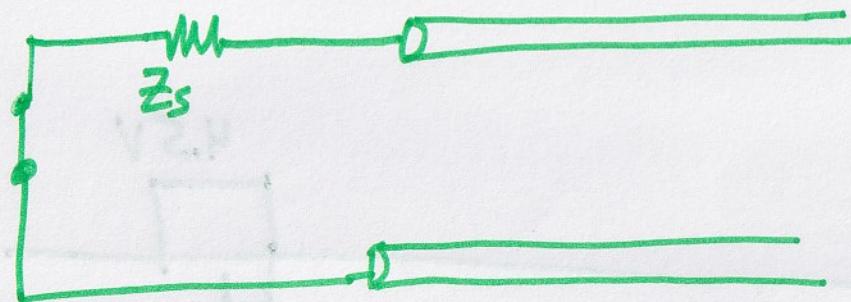


well now, Γ_s this is the reflection coefficient at the source end of the Line

$$\Gamma_s = \frac{Z_s - Z_0}{Z_s + Z_0}$$

$Z_0 = Z_s$ we have a 'Load match' for the problem


$$\text{so } \Gamma_s = 0$$

L4


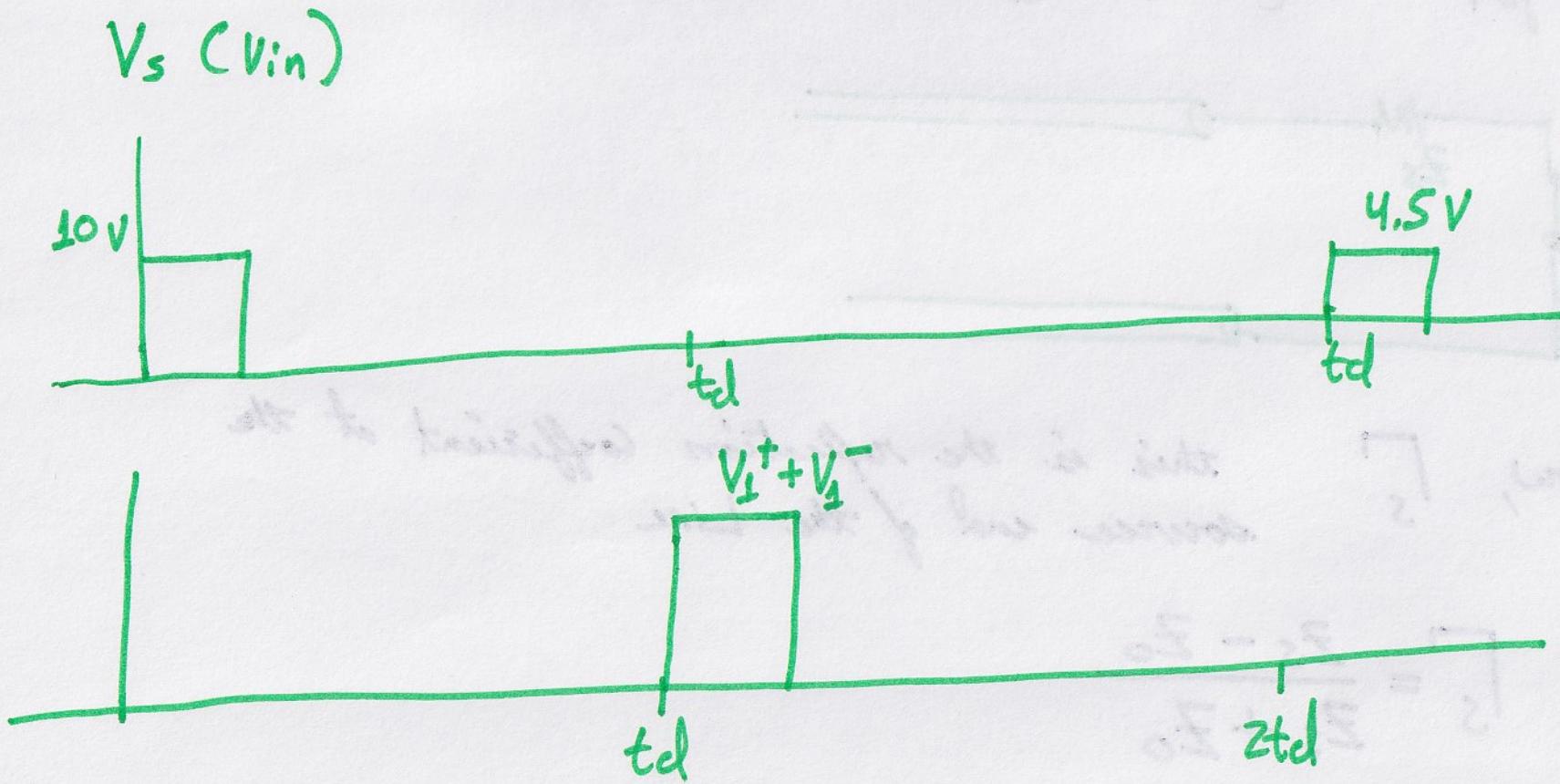


The reflected pulse comes back to hit the source at $2t_d$
(4.5V reflected reflected to the source)

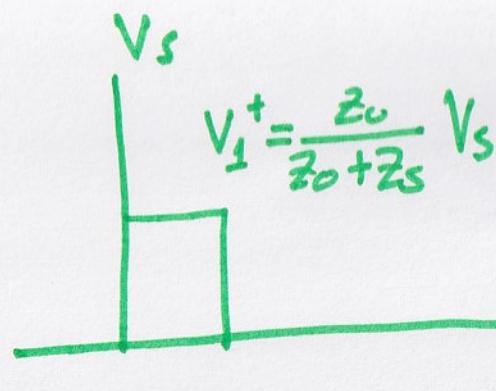as $Z_s = 0$ there is no reflected Voltage to the Load


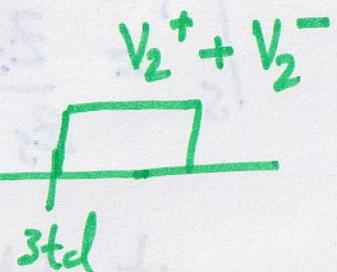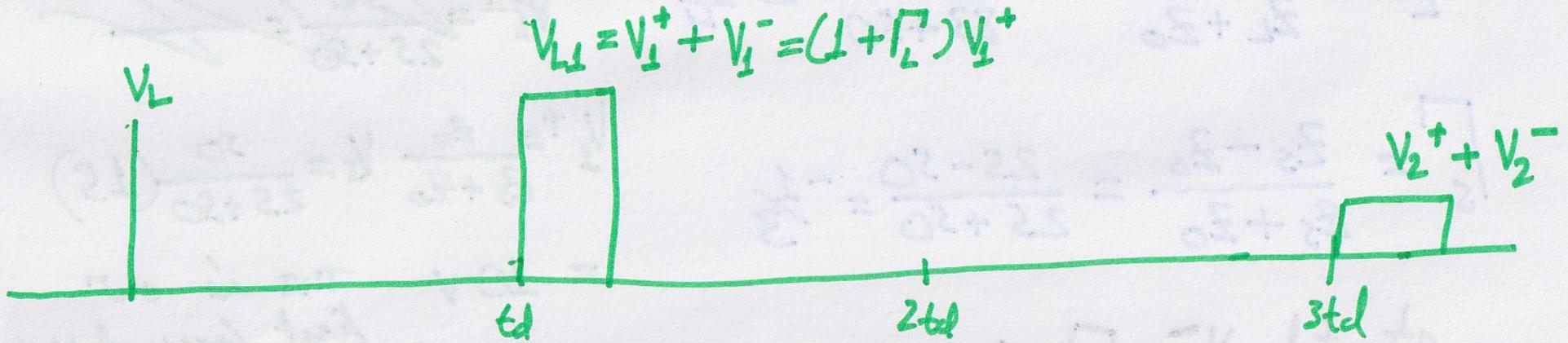
$$\begin{aligned} V_1^- + V_1^+ &= \Gamma_L V_1^+ + \Gamma_S V_1^- \\ &= \Gamma_L V_1^+ + \frac{1}{2} (\Gamma_L V_1^+) \\ &= (\Gamma_L + \Gamma_S \Gamma_L) V_1^+ \end{aligned}$$



(16)

Another Example

$$Z_0 = 50 \Omega, Z_L = 83 \Omega, Z_S = 25$$

$$V_S = 15V$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{83 - 50}{83 + 50} = \frac{1}{4}$$

~~$$V_I^+ = \frac{50}{25 + 50} = \frac{1}{3}$$~~


$$\Gamma_S = \frac{Z_S - Z_0}{Z_S + Z_0} = \frac{25 - 50}{25 + 50} = -\frac{1}{3}$$

$$V_I^+ = \frac{Z_0}{Z_S + Z_0} V_S = \frac{50}{25 + 50} (15)$$


$= 10V$ This is our
first forward wave
This is the first
reflected wave

$$\text{at } 2td \quad V_I^+ = \Gamma_S V_I^- = \left(-\frac{1}{3}\right)(2.5) \approx -0.83 \quad \text{This is the 2nd forward wave}$$

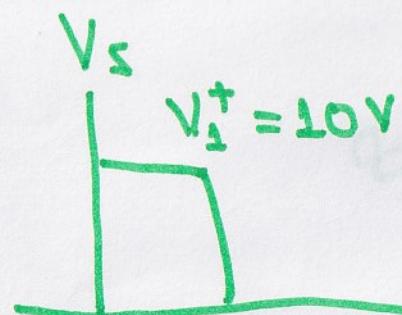
$$\text{at } 3td \quad V_I^- = \Gamma_L V_I^+ = \left(\frac{1}{4}\right)(-0.83) \approx -0.21 \quad \text{This is the 2nd reflected wave}$$


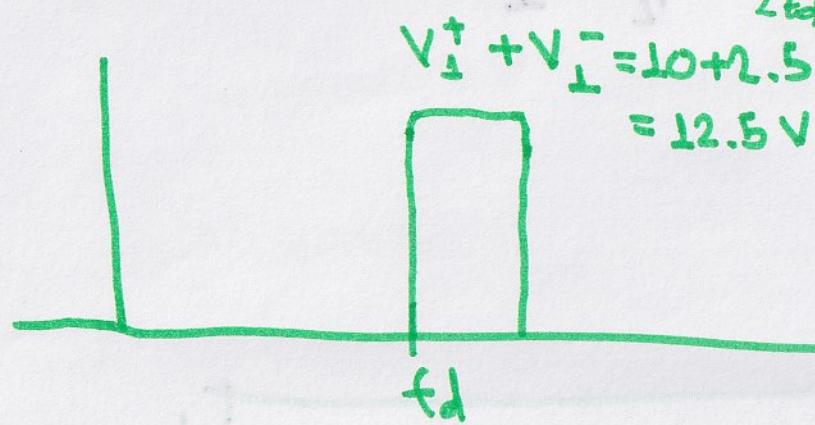
$$V_1^- + V_2^+ = 2.5 - 0.93 = 1.66 \text{ V}$$




$$V_2^+ + V_2^- = -1.04$$

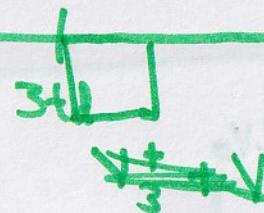

18

Goofy Case Study

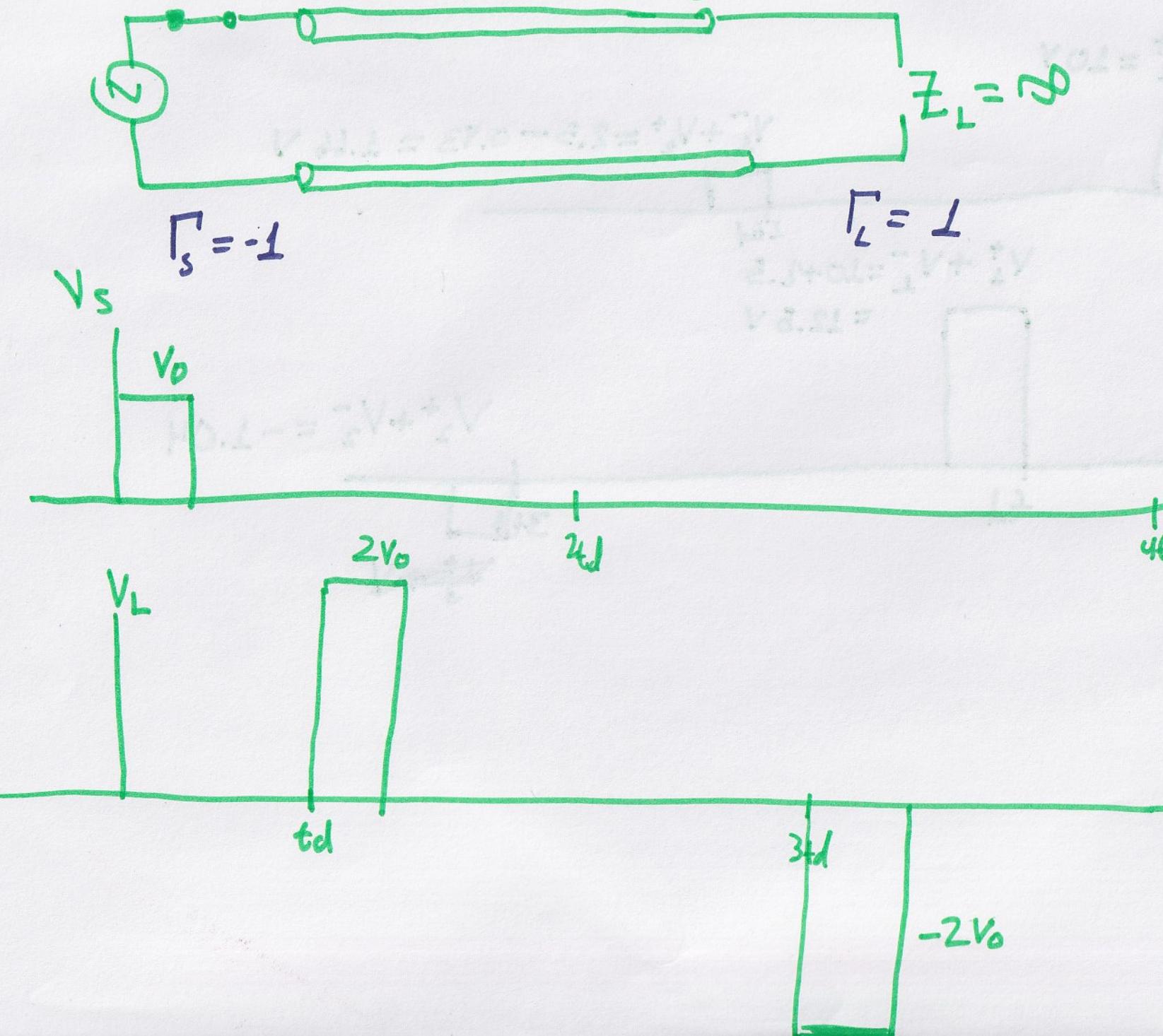


Bounce Diagram (Lattice Diagram)

$$Z_0 = 50, Z_L = 83, Z_S = 25 \quad V_S = 15 \text{ V pulse}$$

$$\Gamma_L = \frac{1}{4} \quad \Gamma_S = -\frac{1}{3}$$

We have another way to look at this

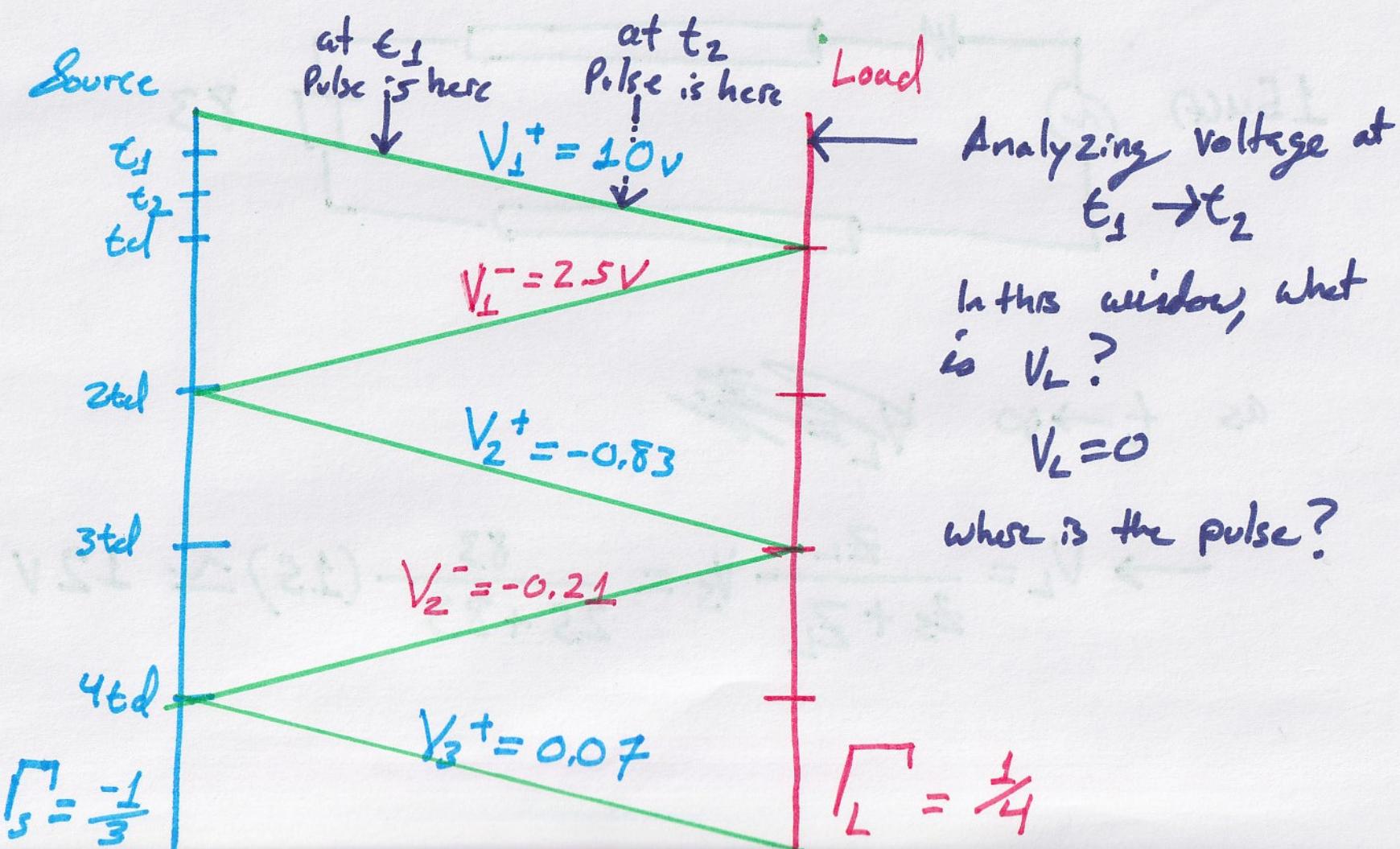


20

Long PulseExample is Step Function

→ turn a switch on and leave it on.

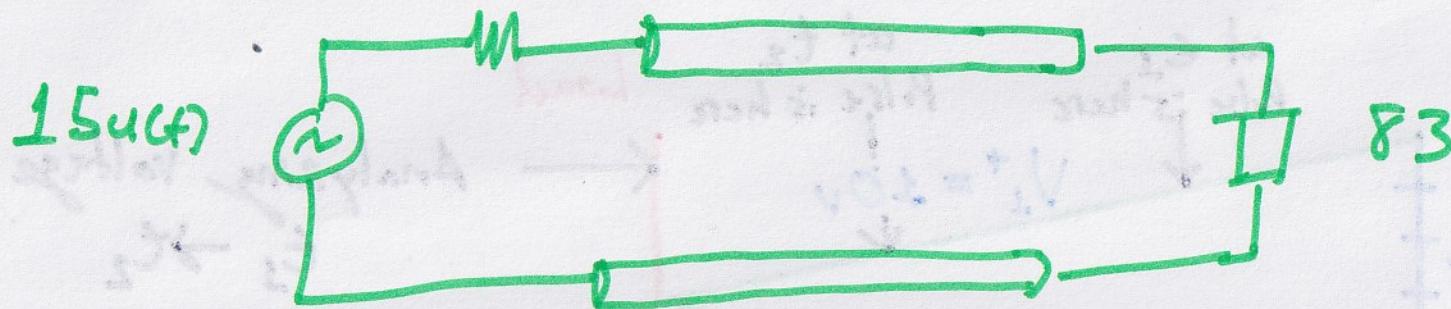$V_s = 15 \text{ V}$, turned on at $t=0$ (stays on)




as $t \rightarrow \infty$ ~~$V_L = ?$~~


$$\rightarrow V_L = \frac{Z_L}{Z_S + Z_L} V_s = \frac{83}{25 + 83} (15) \approx 12 \text{ V}$$

Here's how this happens

21

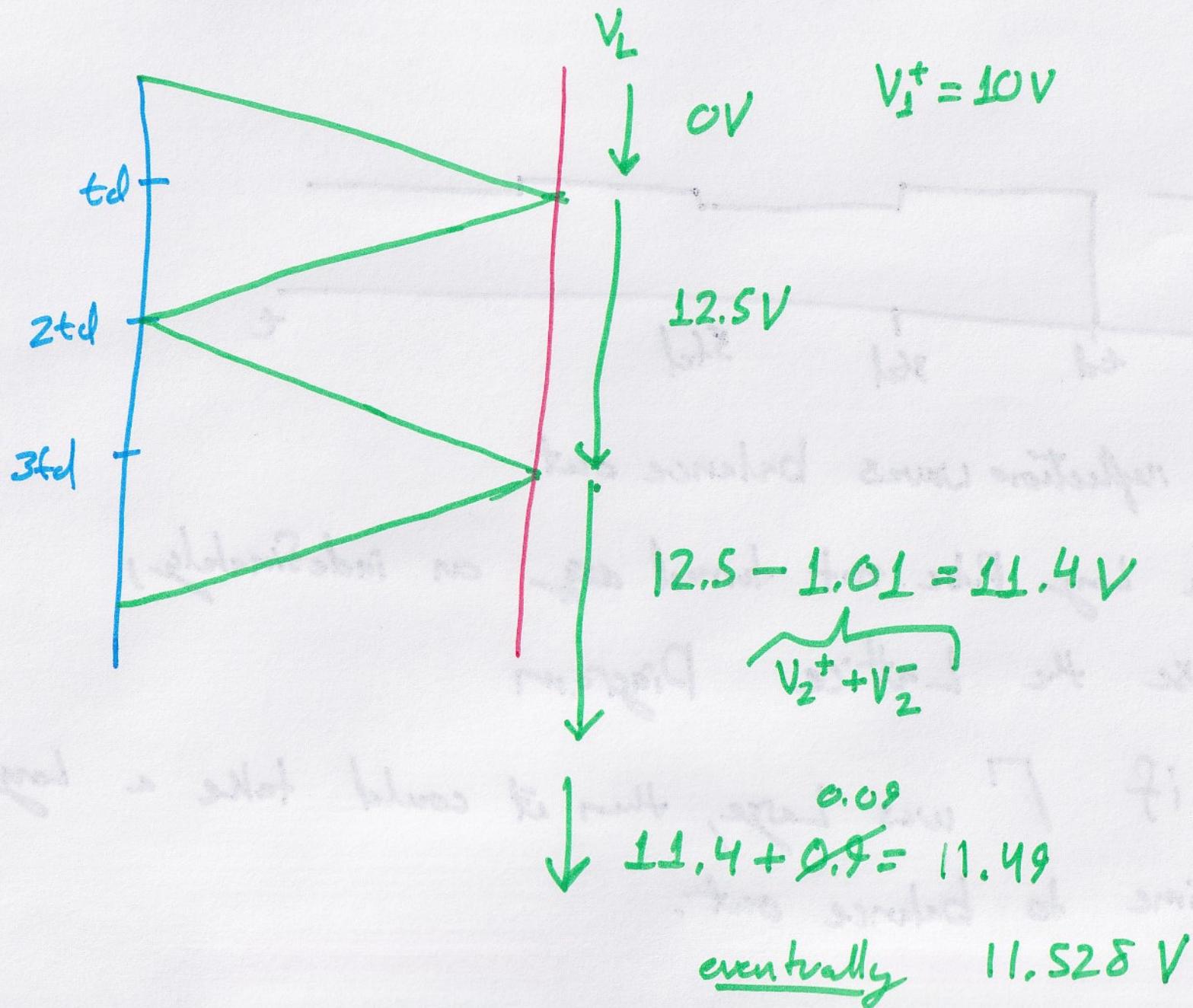

(22) Eventually we converge to DC value

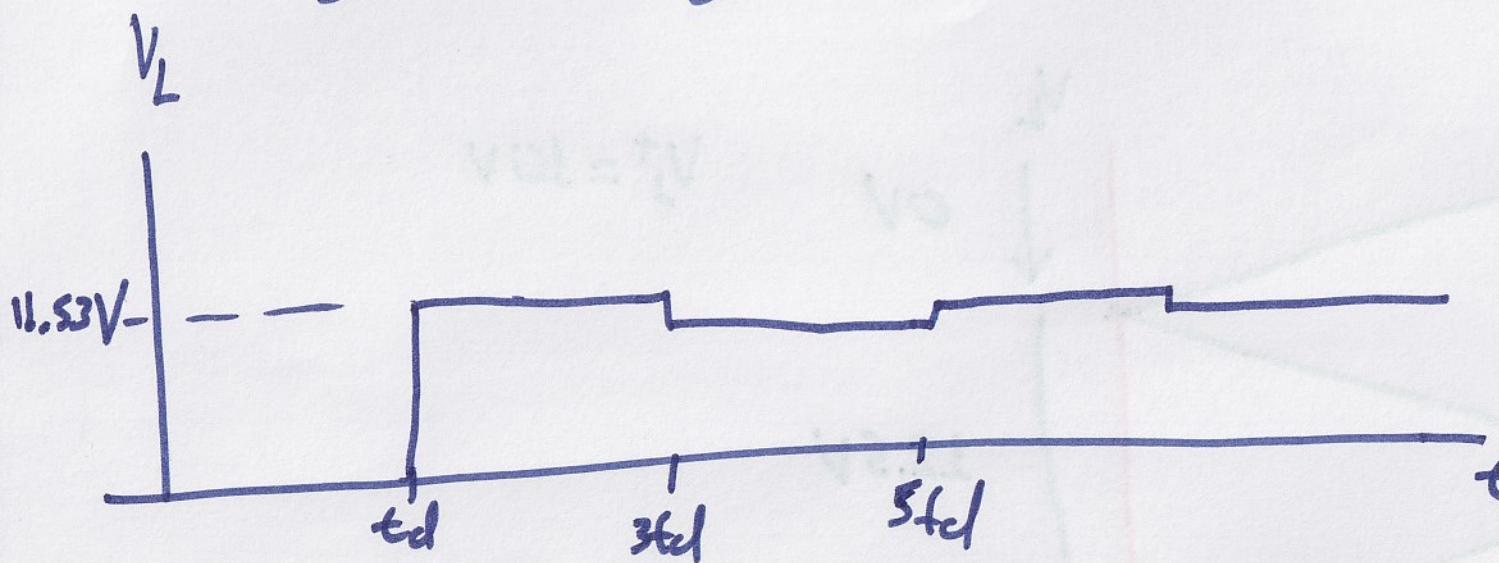

The reflection waves balance out

For a Long Pulse not turned off on indefinitely,
use the Lattice Diagram

if Γ was Large, then it could take a long
time to balance out.